

cdr@wp.pl




1998 Audi A6



SYSTEM WIRING DIAGRAMS

Ground Distribution Circuit (1 of 2)


1998 Audi A6

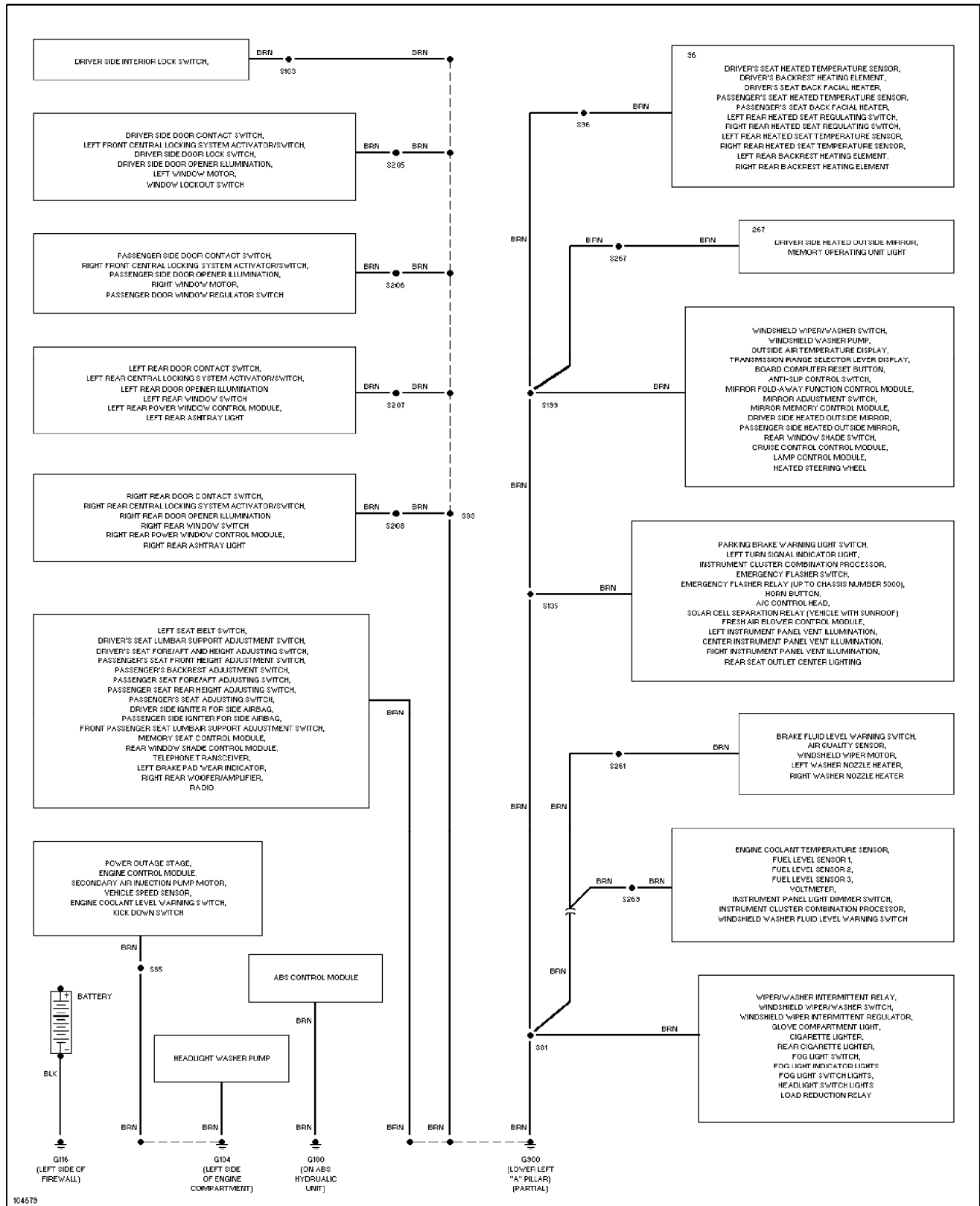

SYSTEM WIRING DIAGRAMS

Ground Distribution Circuit (2 of 2)


1998 Audi A6

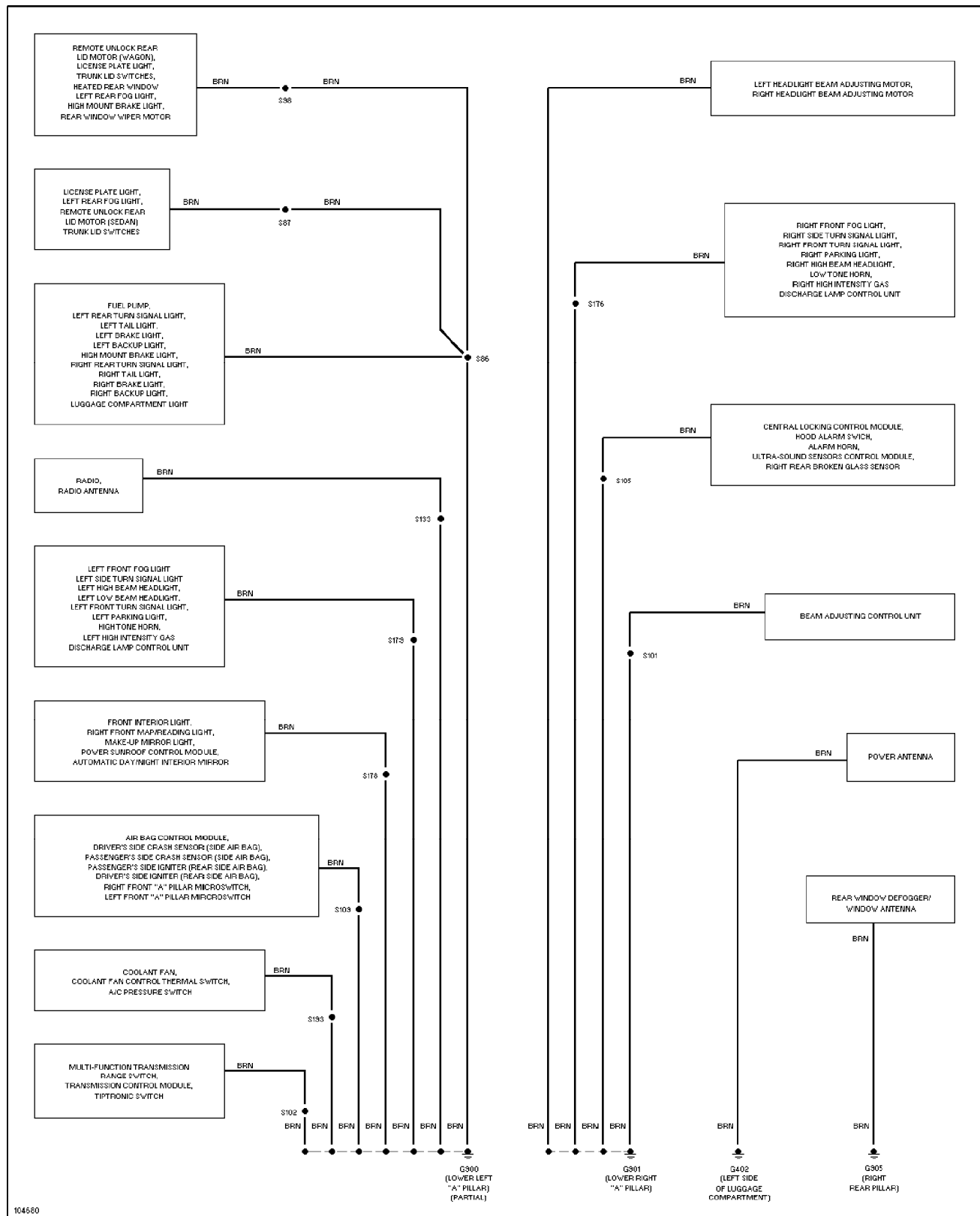

SYSTEM WIRING DIAGRAMS

Air Conditioning Circuits (2 of 2)

1998 Audi A6

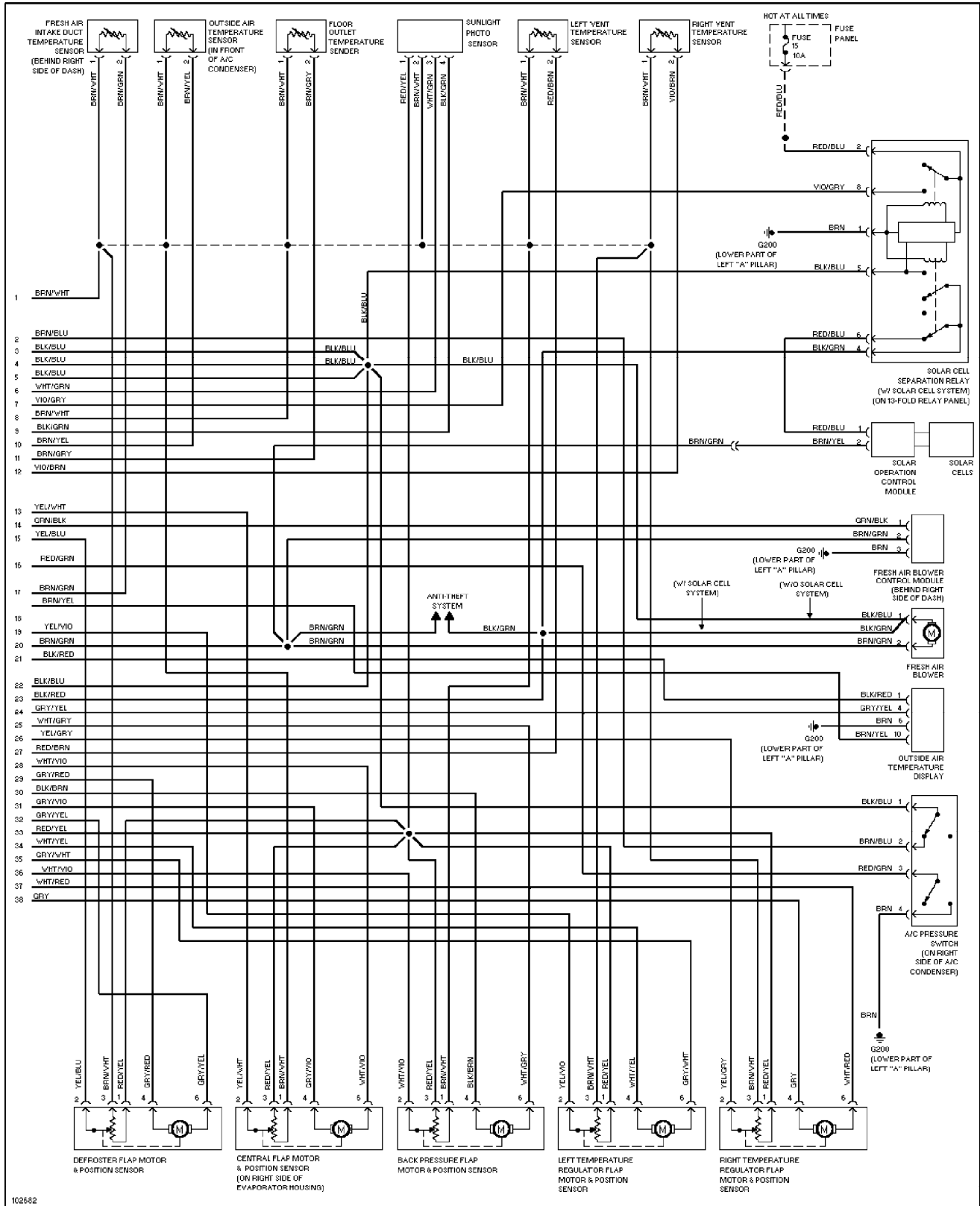


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Anti-theft Circuit (1 of 2)


1998 Audi A6

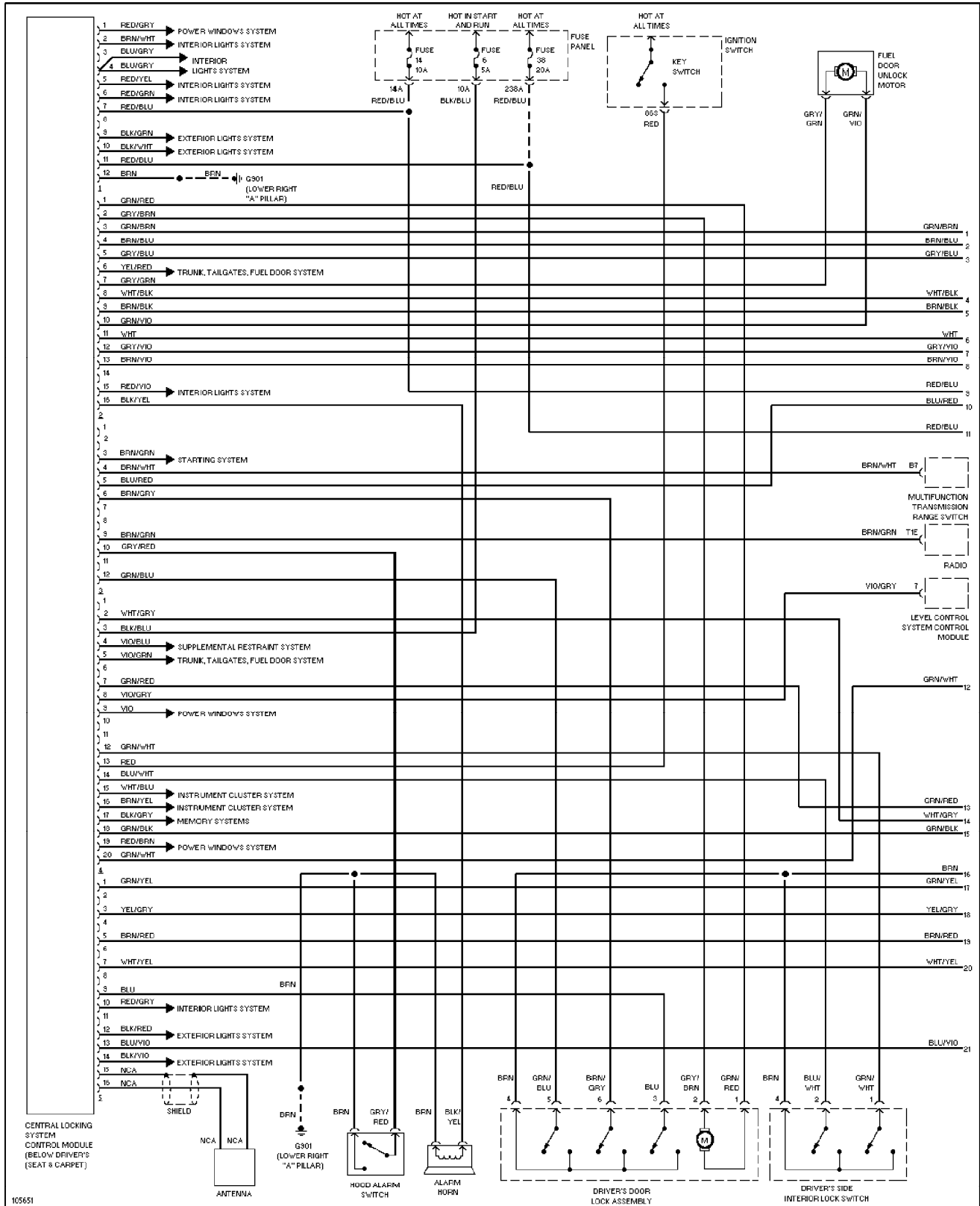

SYSTEM WIRING DIAGRAMS

Anti-theft Circuit (2 of 2)


1998 Audi A6

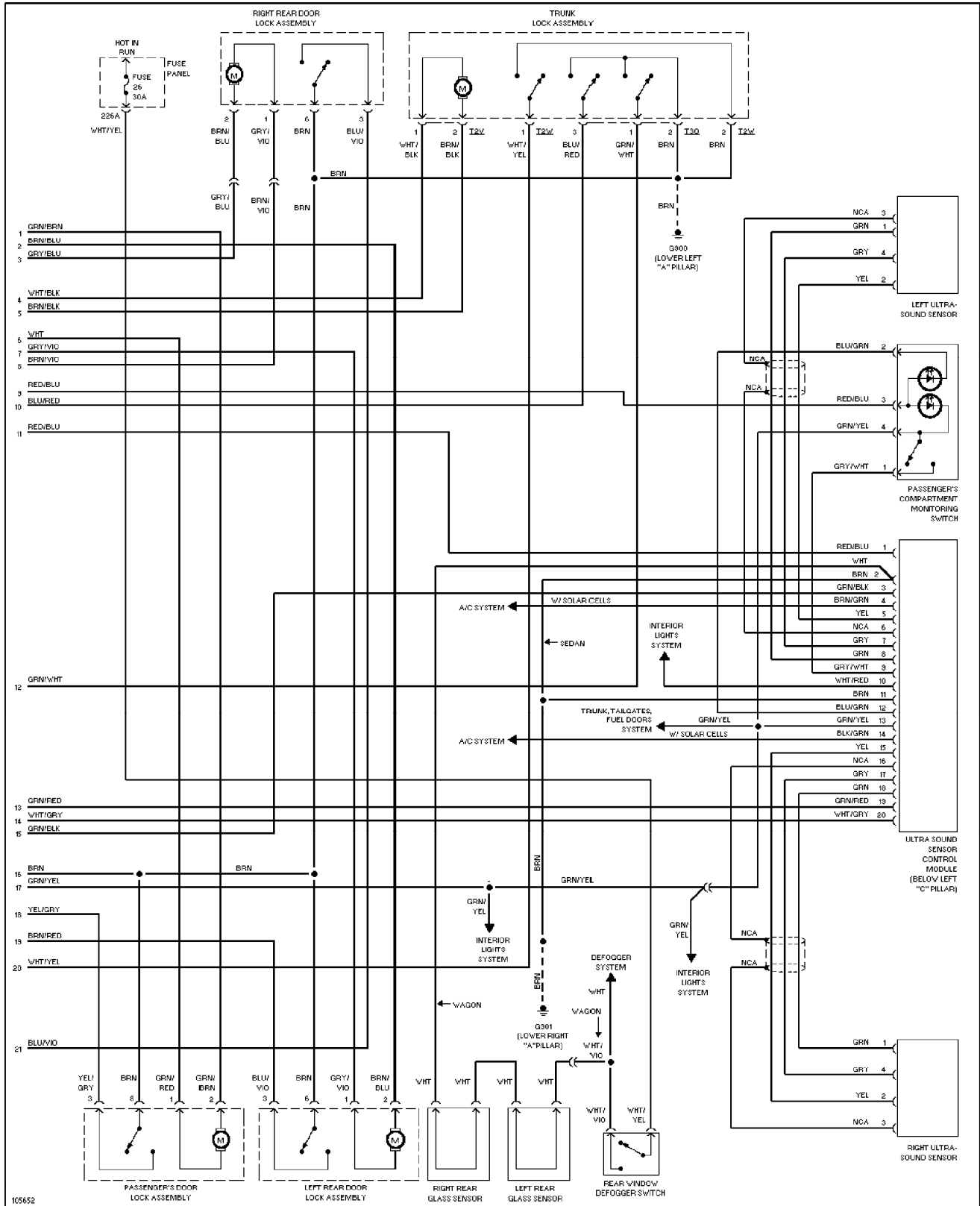

SYSTEM WIRING DIAGRAMS

Computer Data Lines

1998 Audi A6

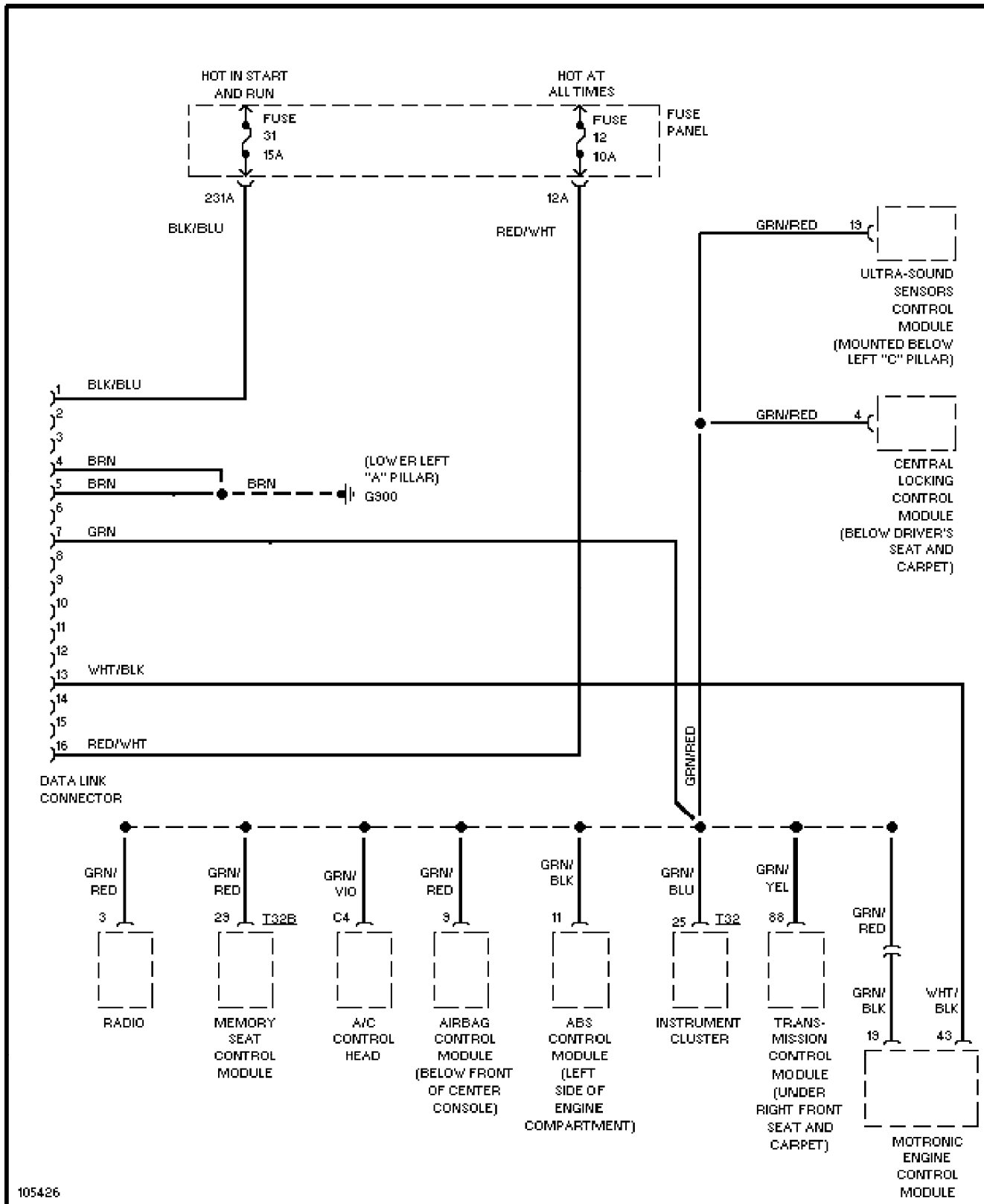


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Cruise Control Circuit


1998 Audi A6

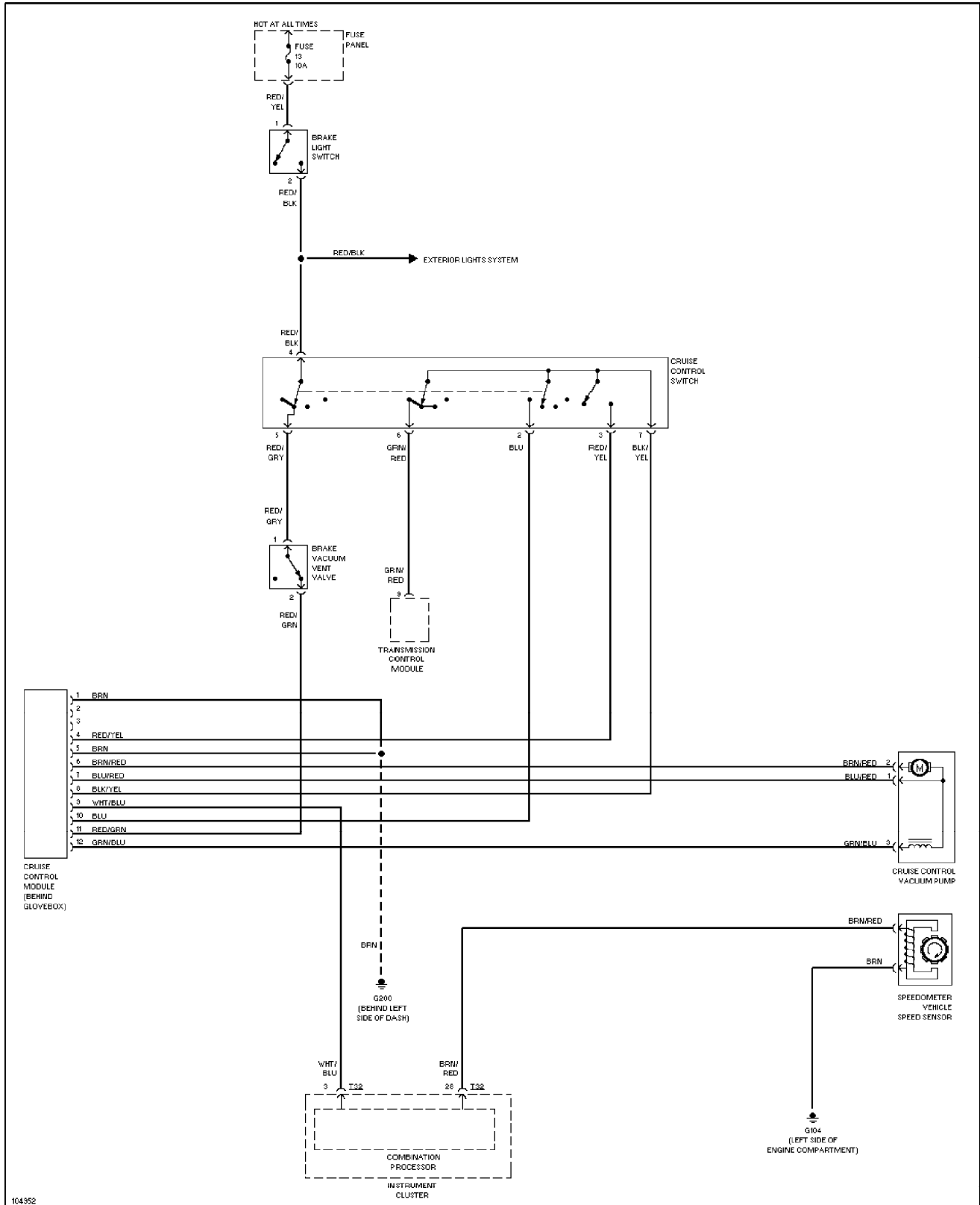


SYSTEM WIRING DIAGRAMS

Defogger Circuit

1998 Audi A6

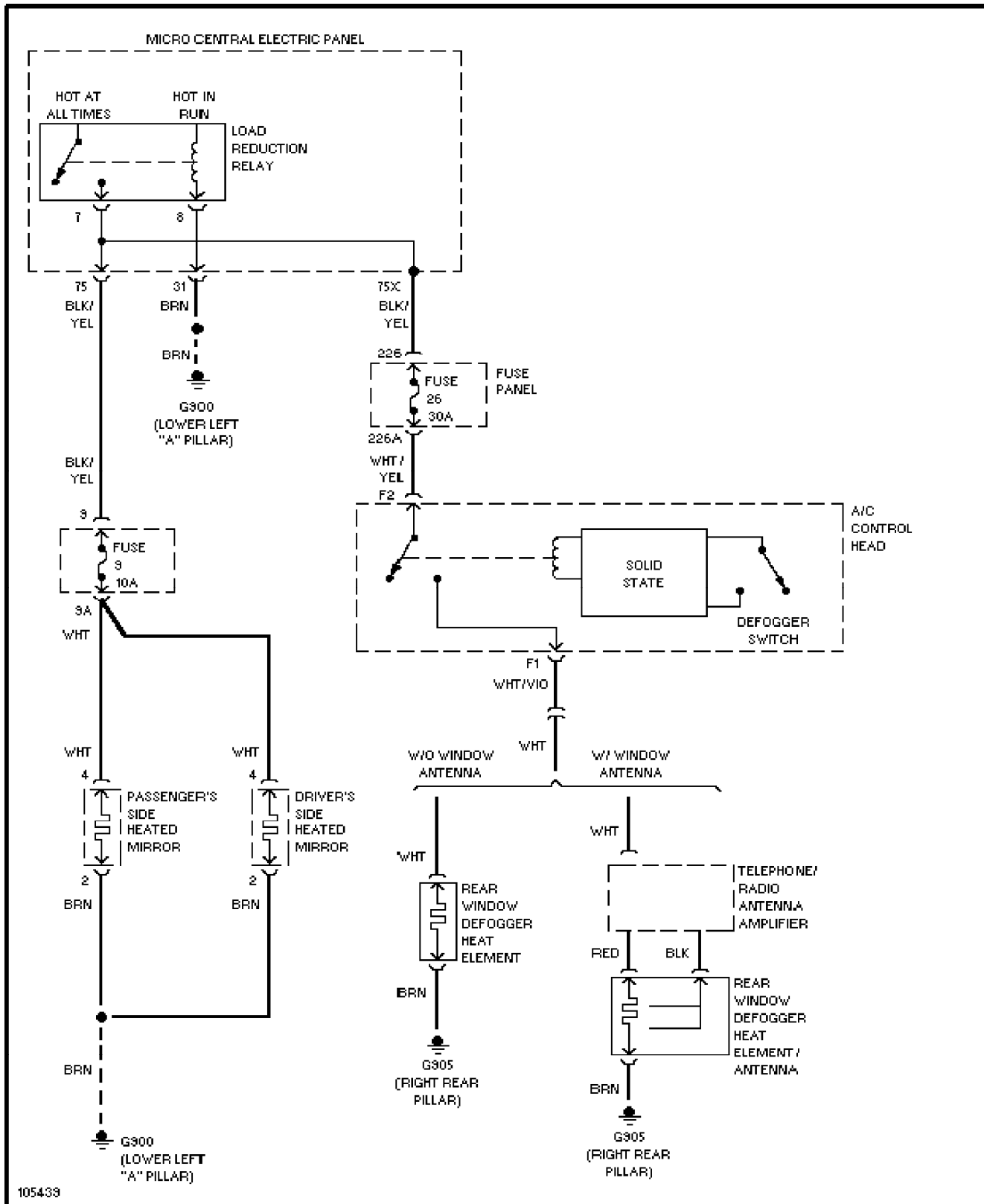

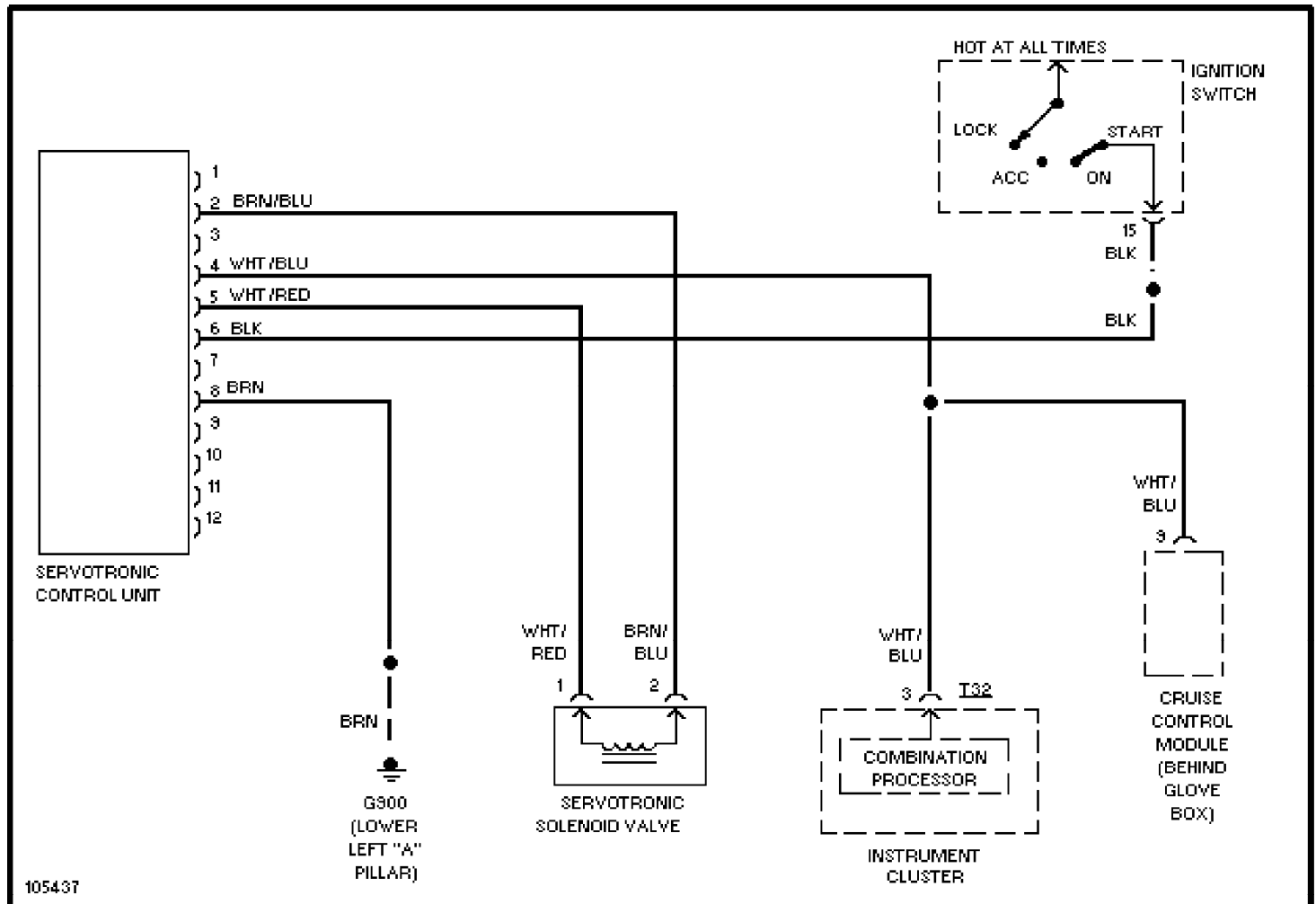
SYSTEM WIRING DIAGRAMS
Electronic Power Steering Circuit
1998 Audi A6



SYSTEM WIRING DIAGRAMS

2.8L, Engine Performance Circuits (1 of 2)

1998 Audi A6

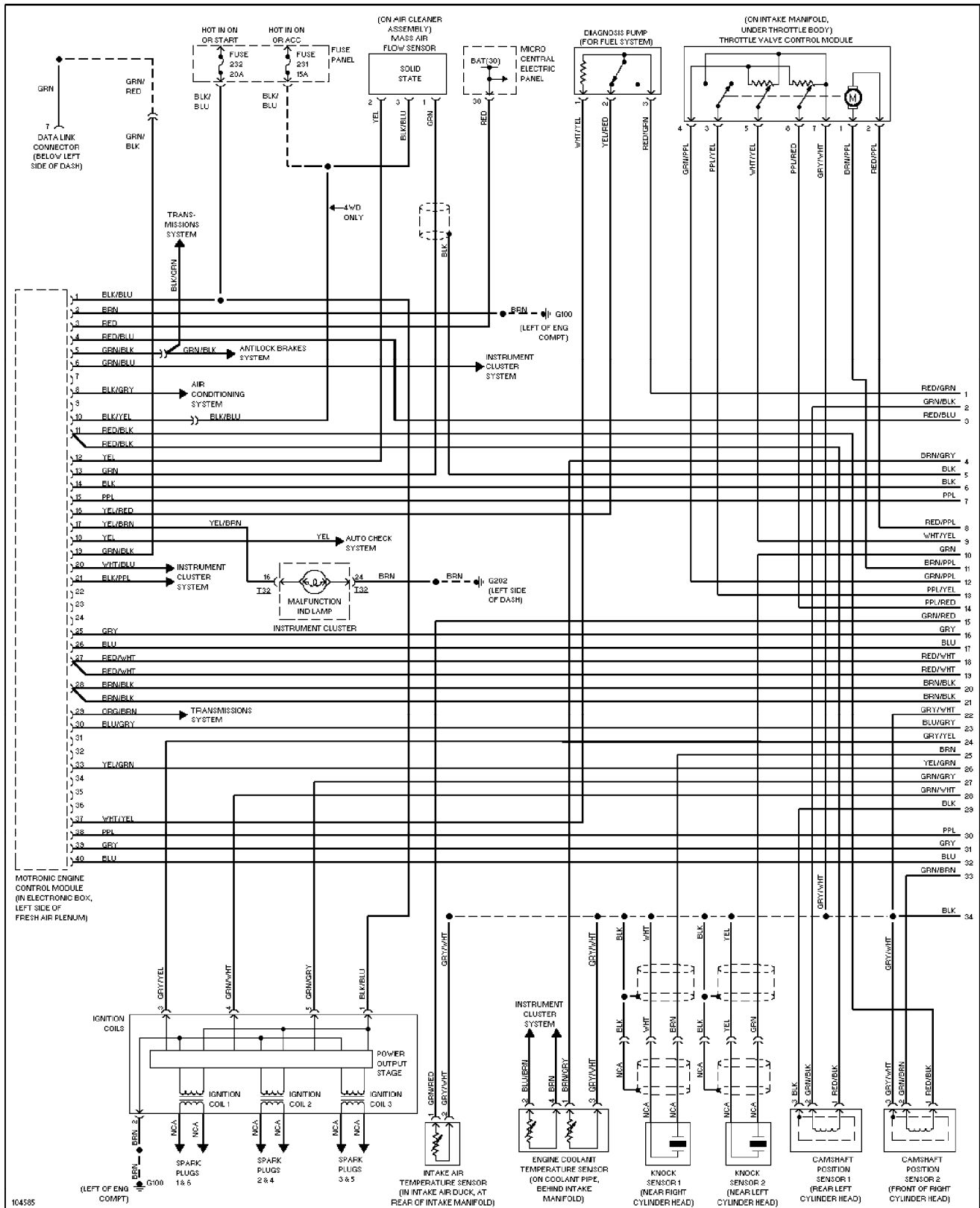


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Back-up Lamps Circuit

1998 Audi A6

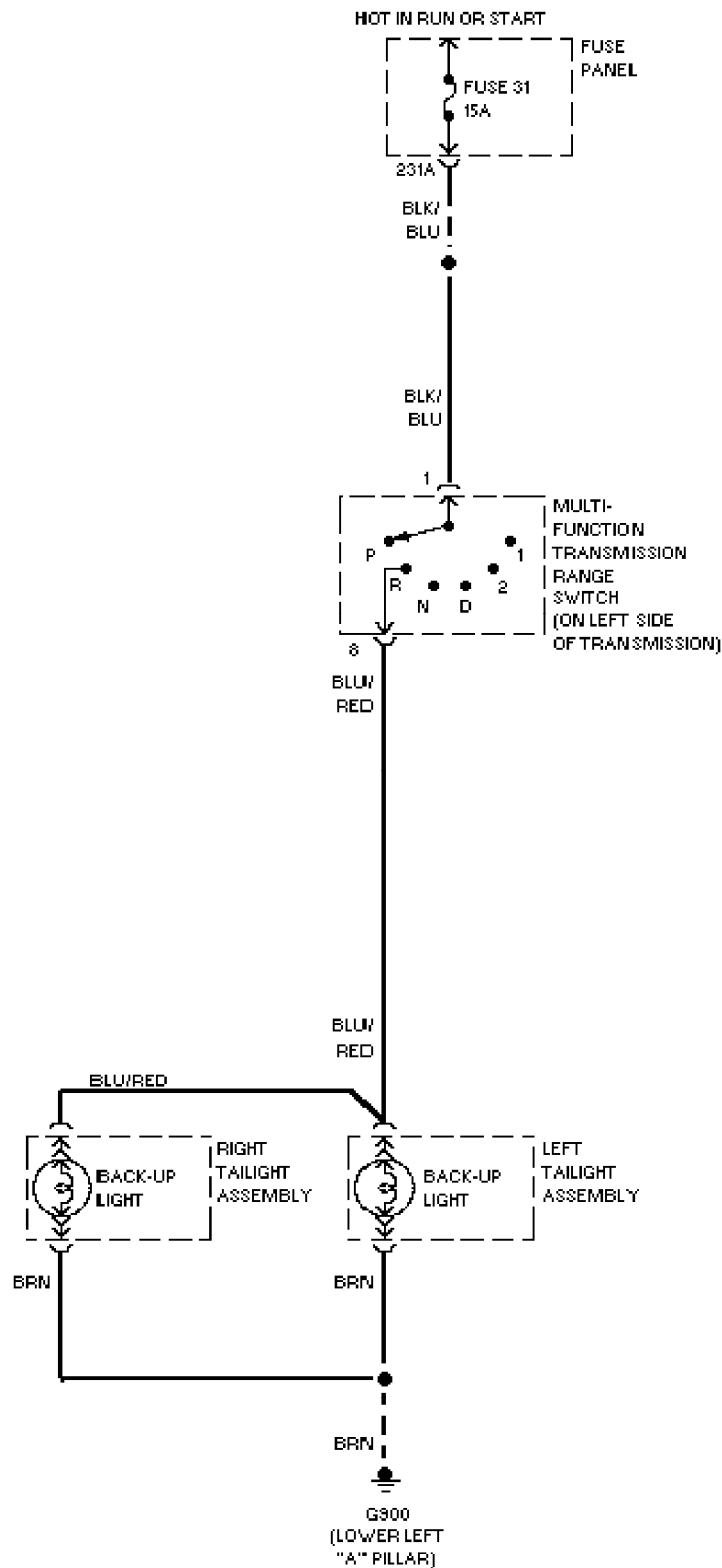


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Exterior Lamps Circuit, W/ DRL & Chassis Number from 5001


1998 Audi A6

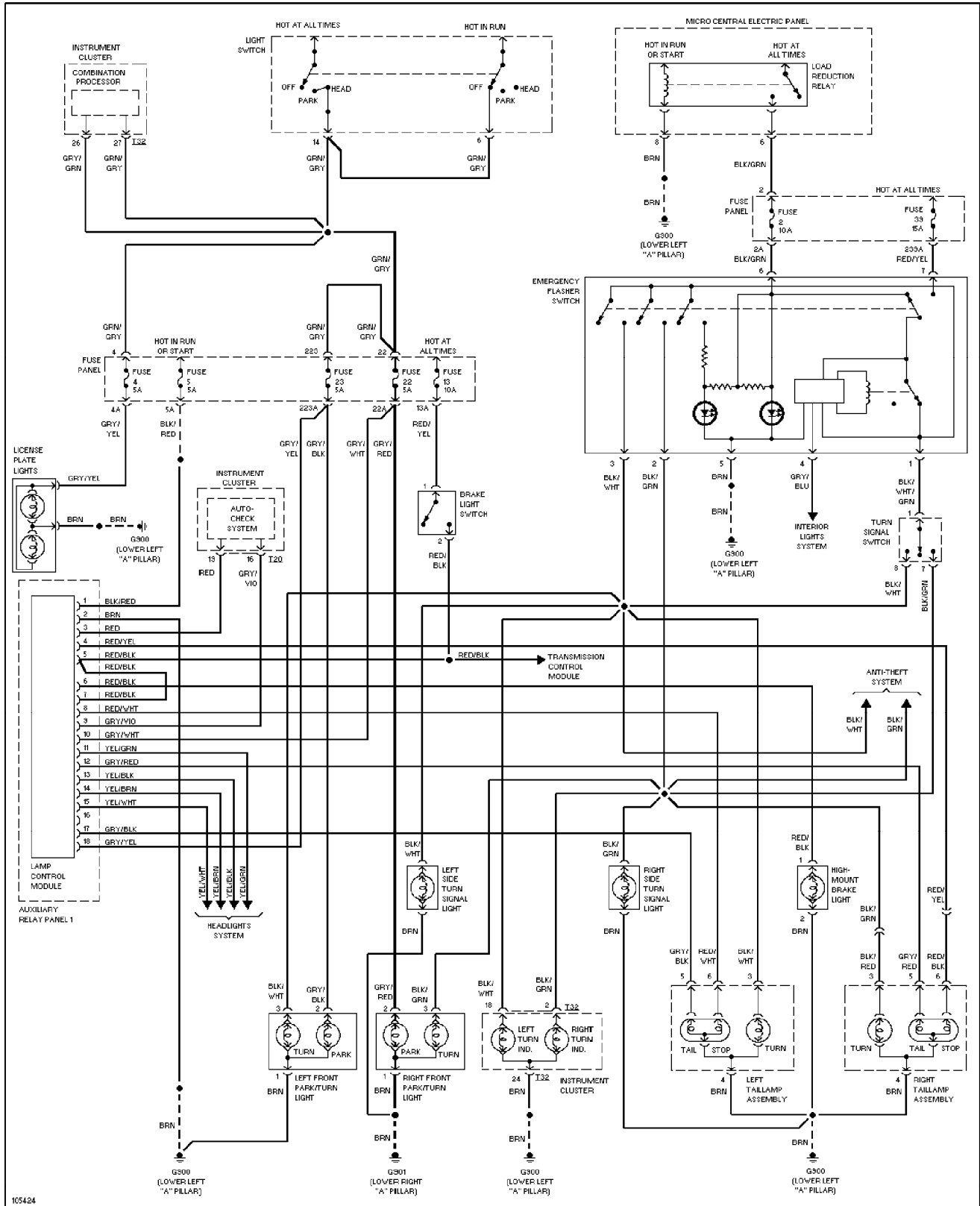

SYSTEM WIRING DIAGRAMS

Air Conditioning Circuits (1 of 2)


1998 Audi A6

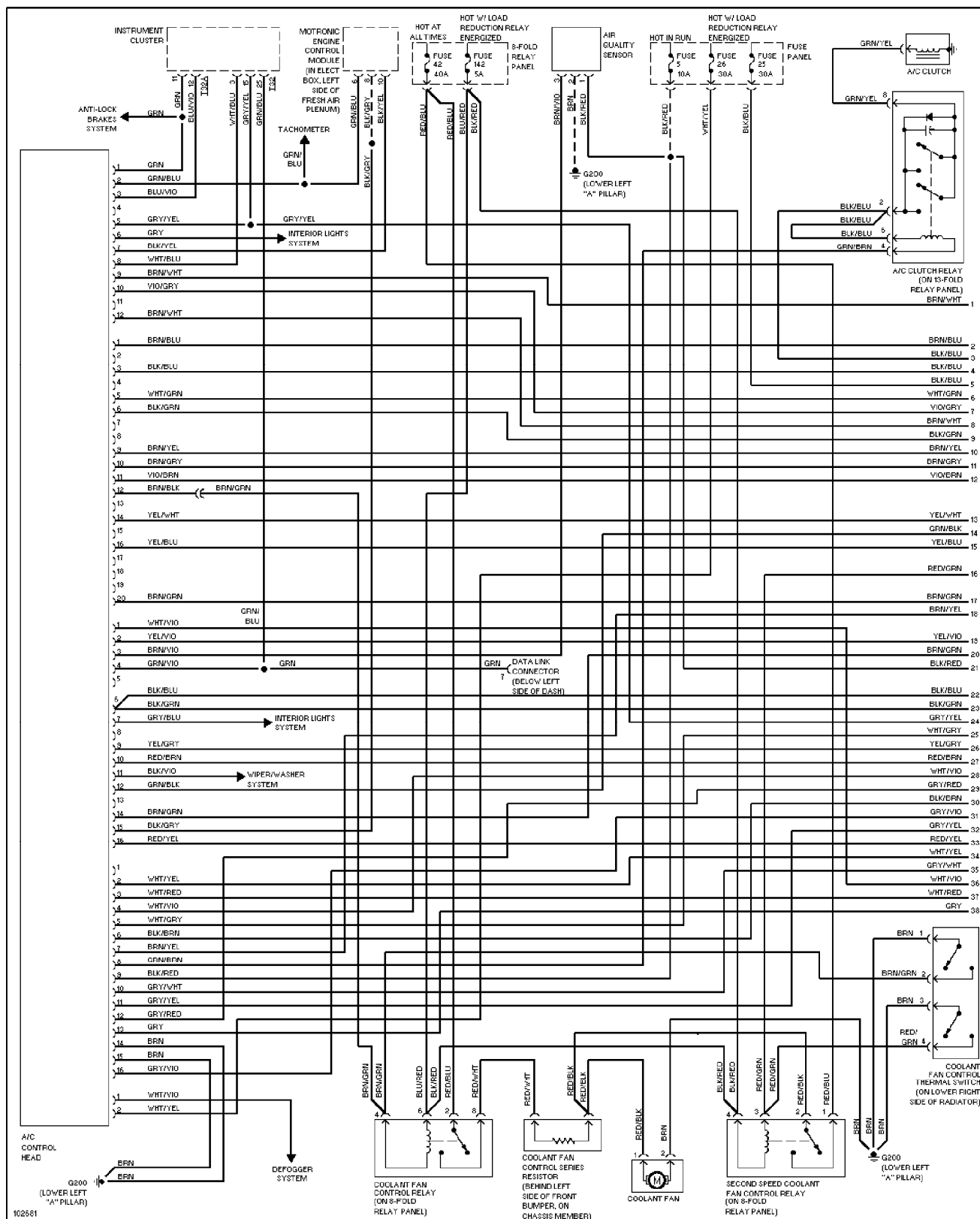

SYSTEM WIRING DIAGRAMS

Power Door Lock Circuit (1 of 2)


1998 Audi A6

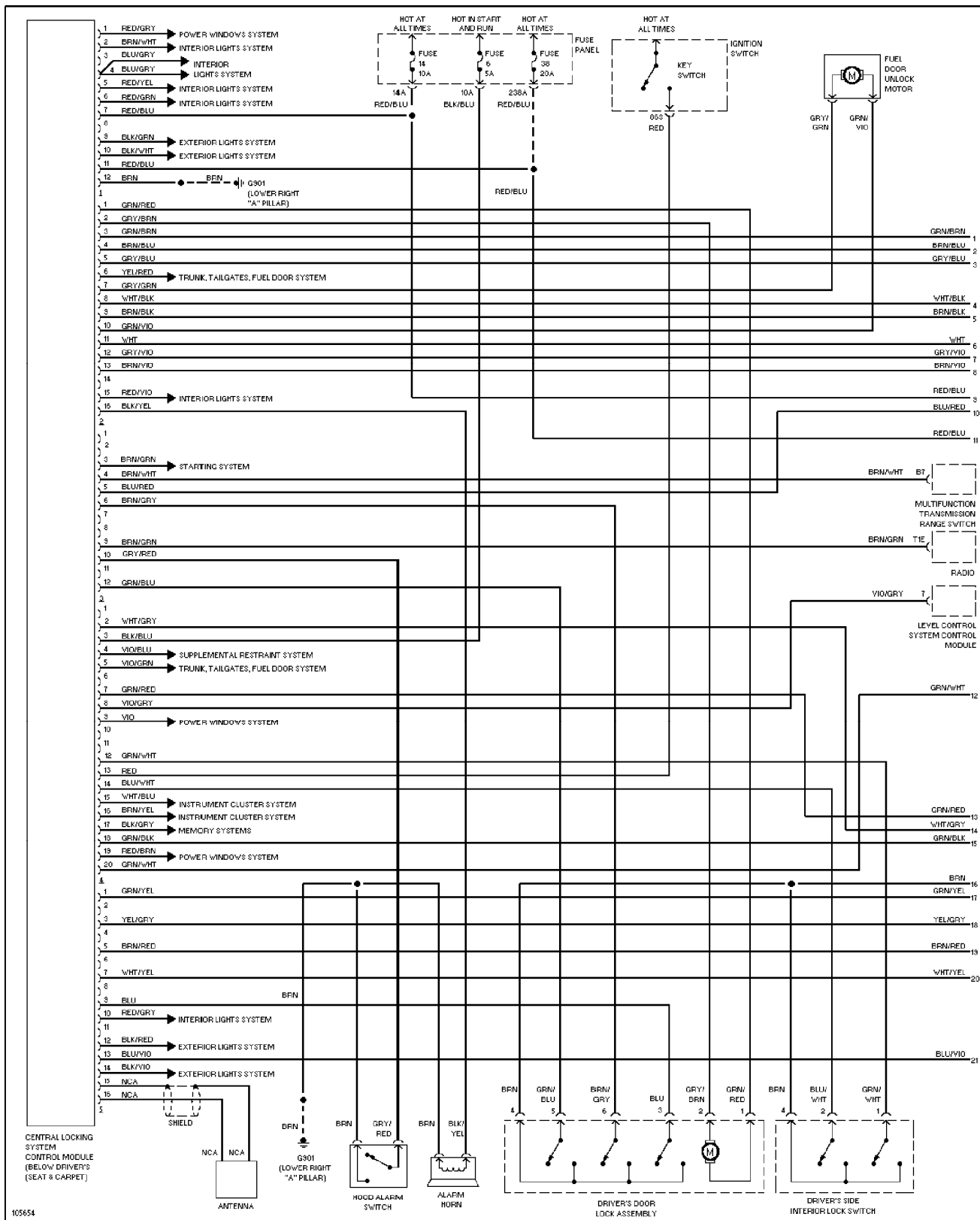


SYSTEM WIRING DIAGRAMS

Trunk Release Circuit

1998 Audi A6

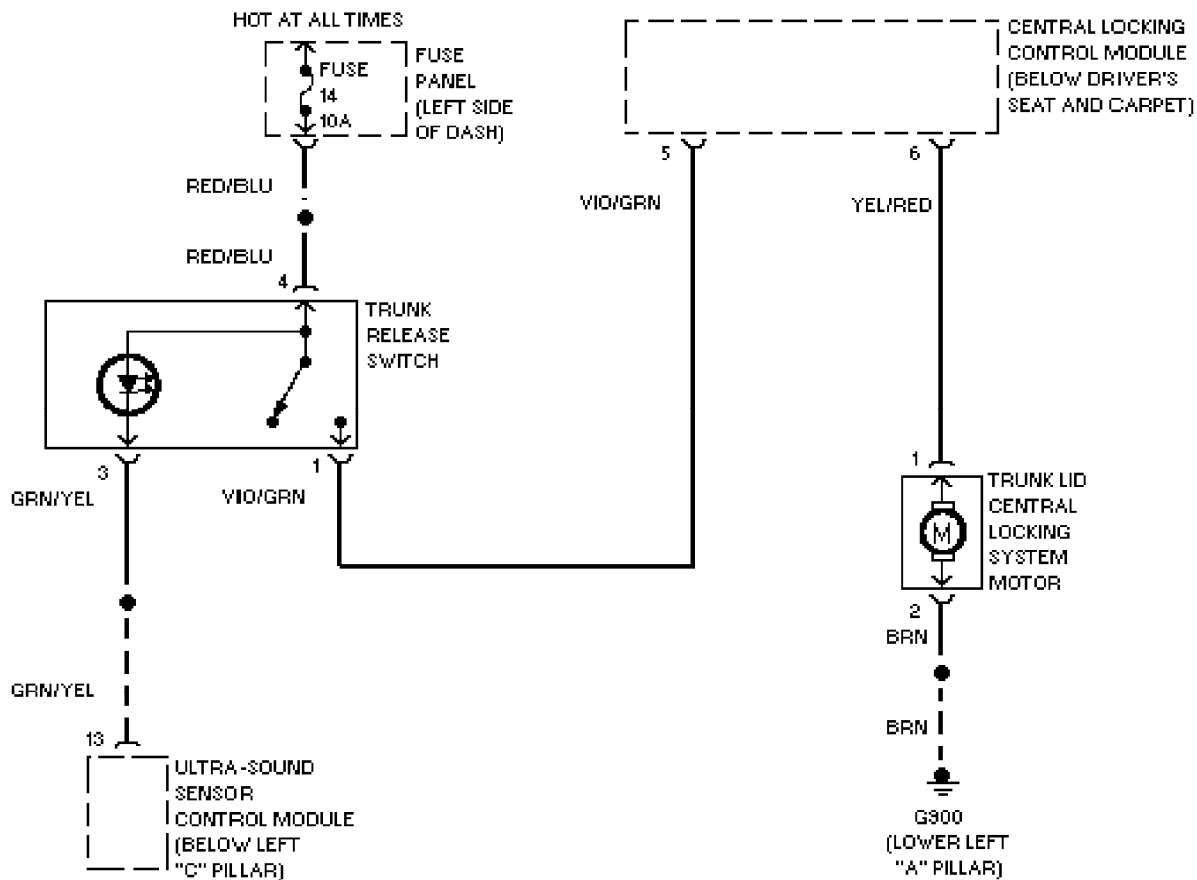


1998 Audi A6

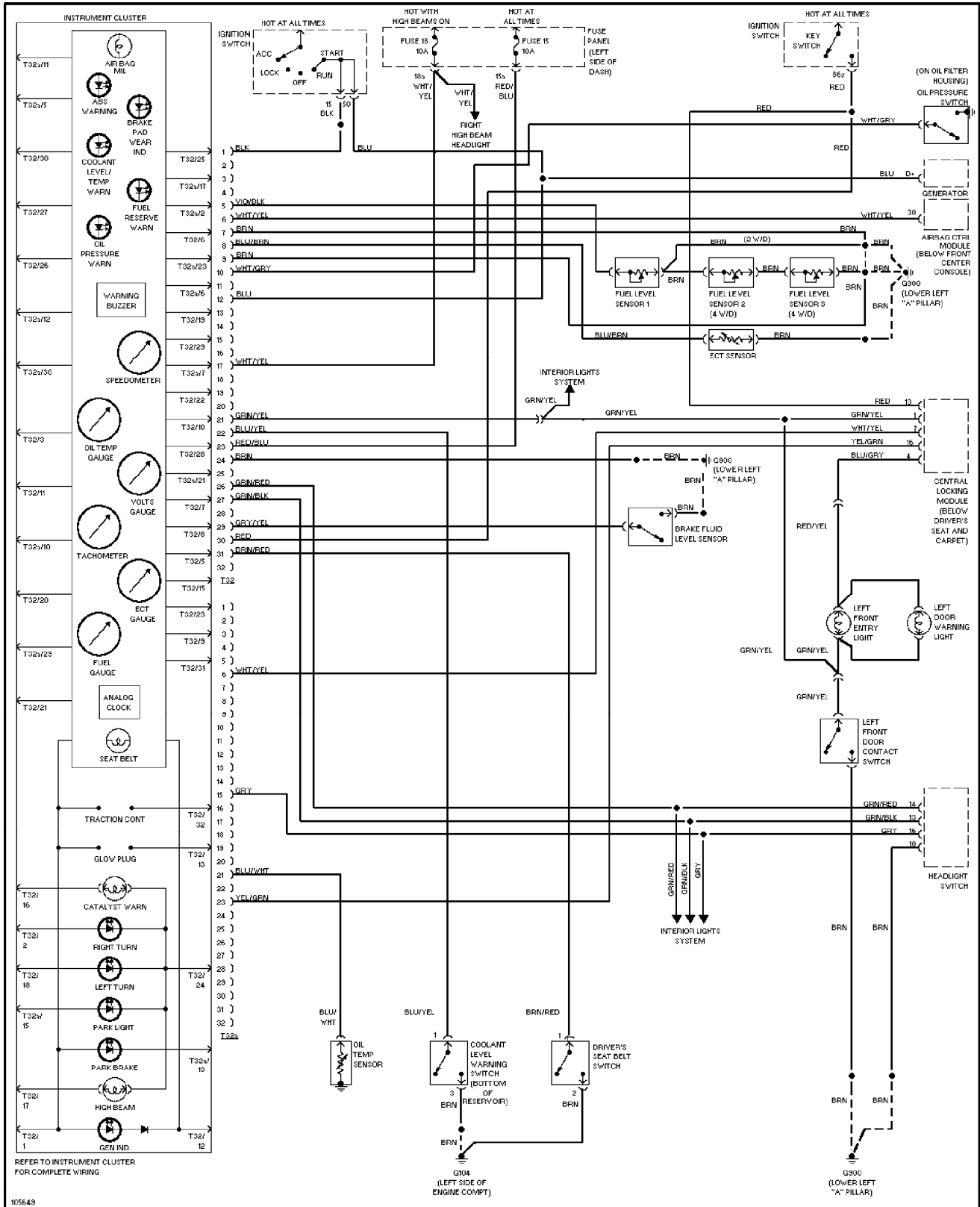

SYSTEM WIRING DIAGRAMS

Wiper/Washer Circuit


1998 Audi A6

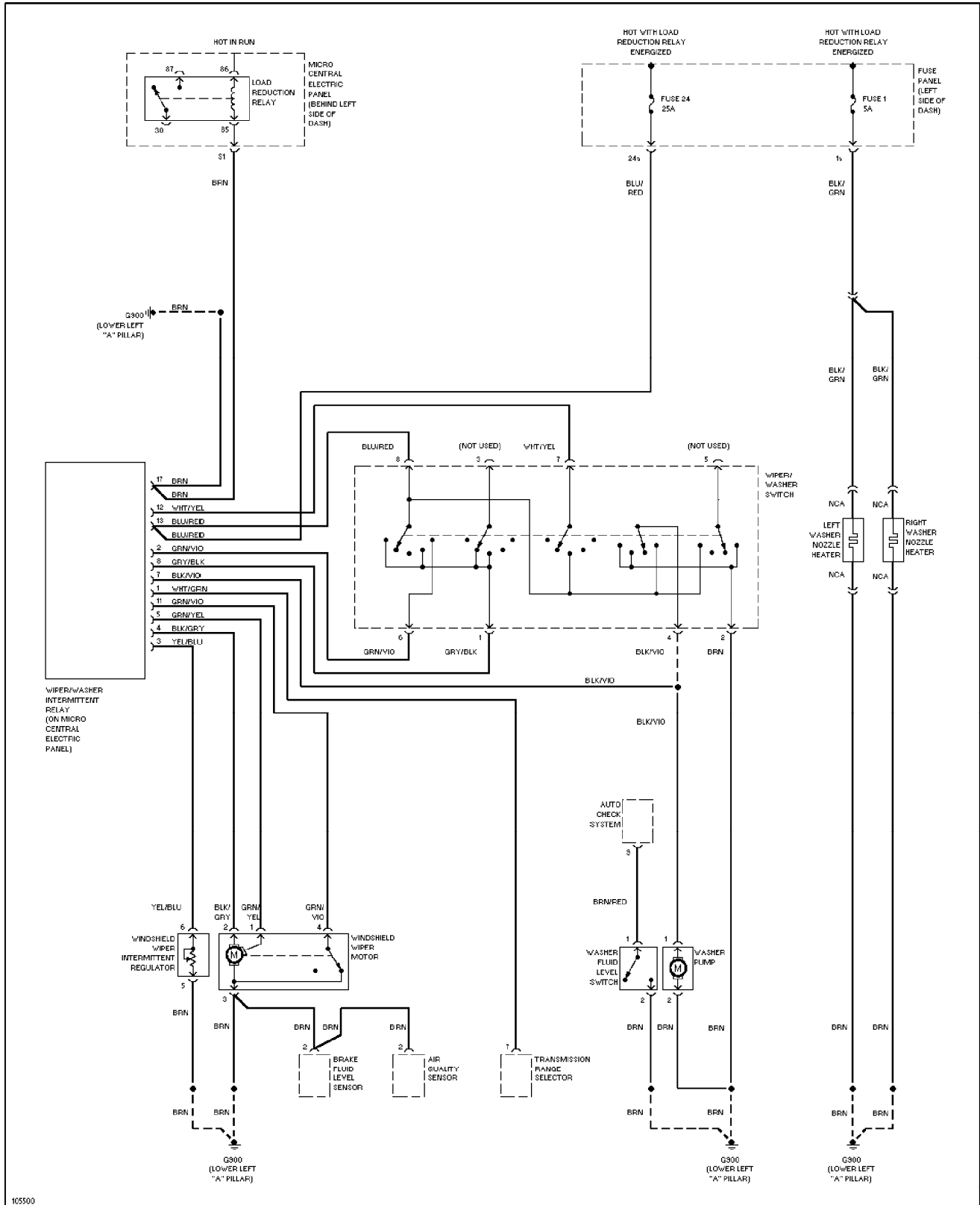

SYSTEM WIRING DIAGRAMS

Heated Seats Circuit


1998 Audi A6

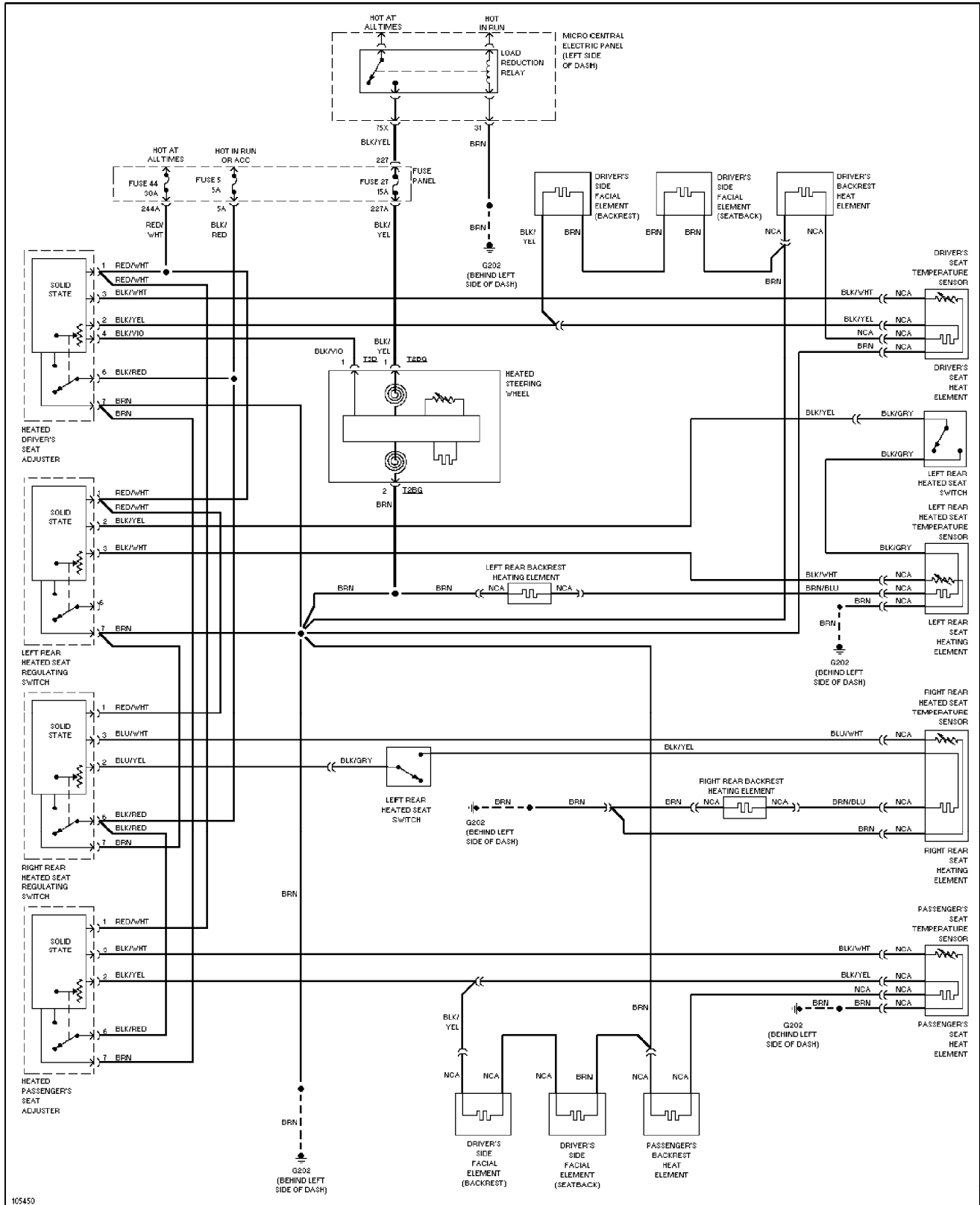

SYSTEM WIRING DIAGRAMS

Passenger Power Seat Circuit


1998 Audi A6

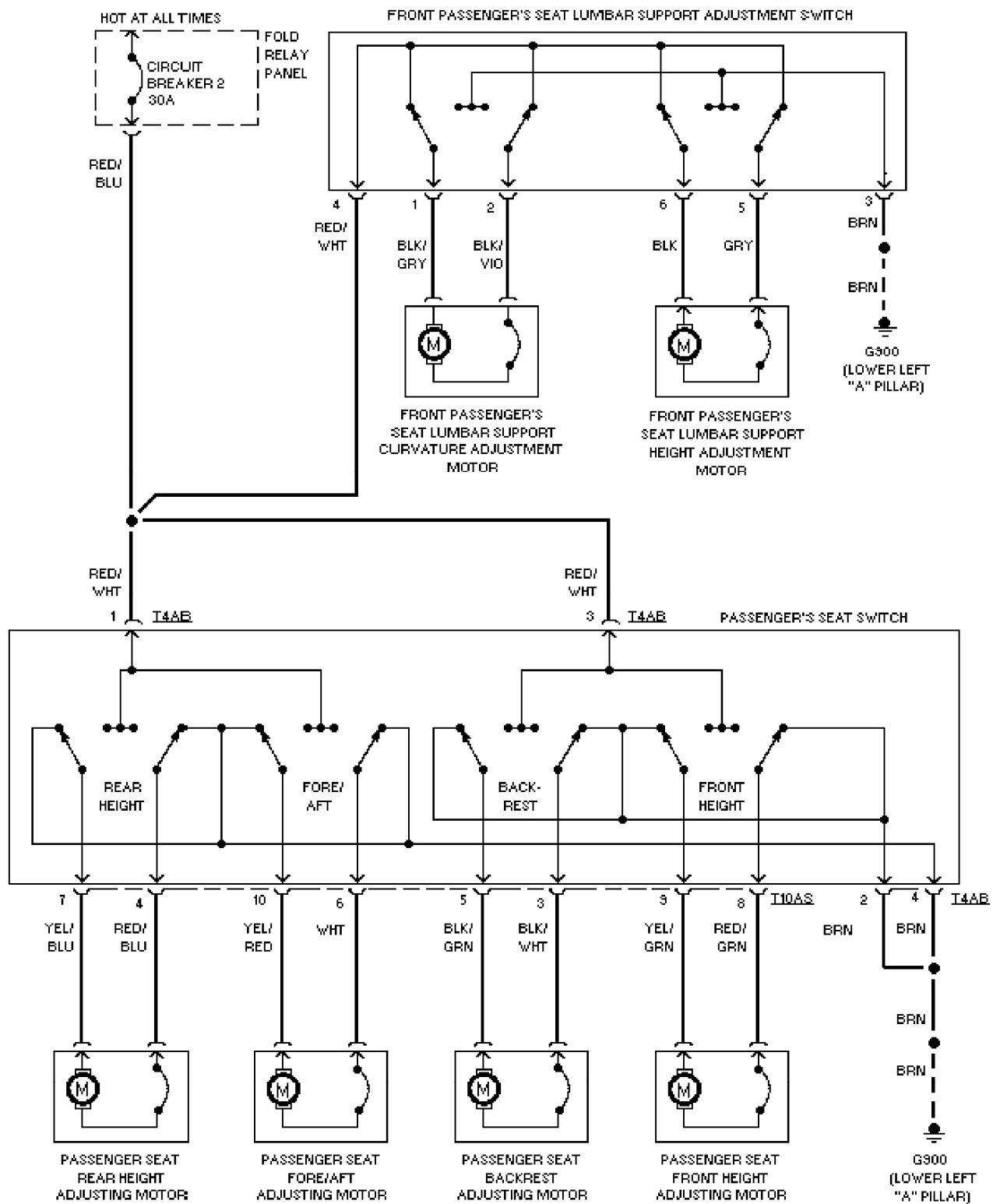

SYSTEM WIRING DIAGRAMS

Power Top/Sunroof Circuits


1998 Audi A6

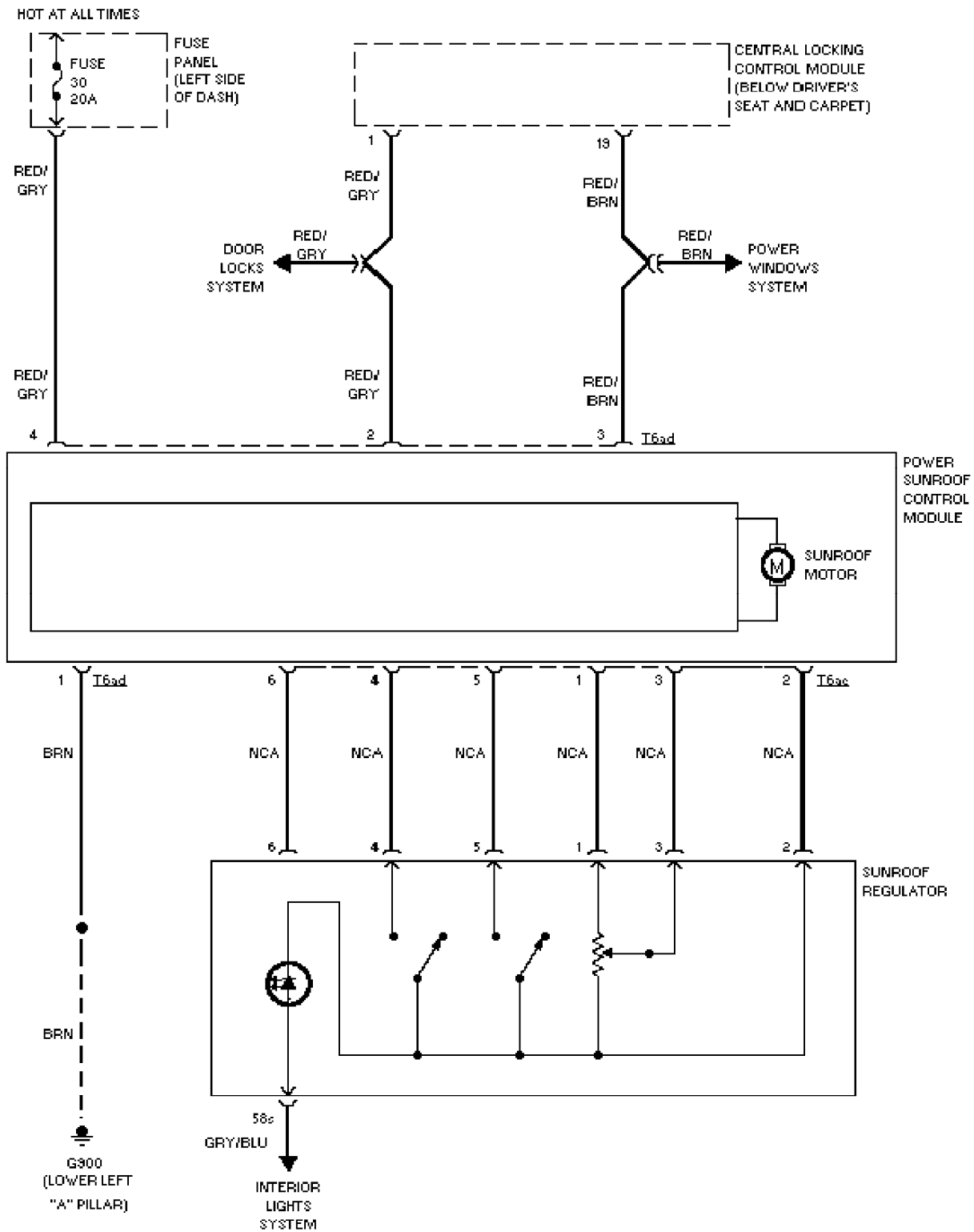

SYSTEM WIRING DIAGRAMS

Power Window Circuit (1 of 2)

1998 Audi A6

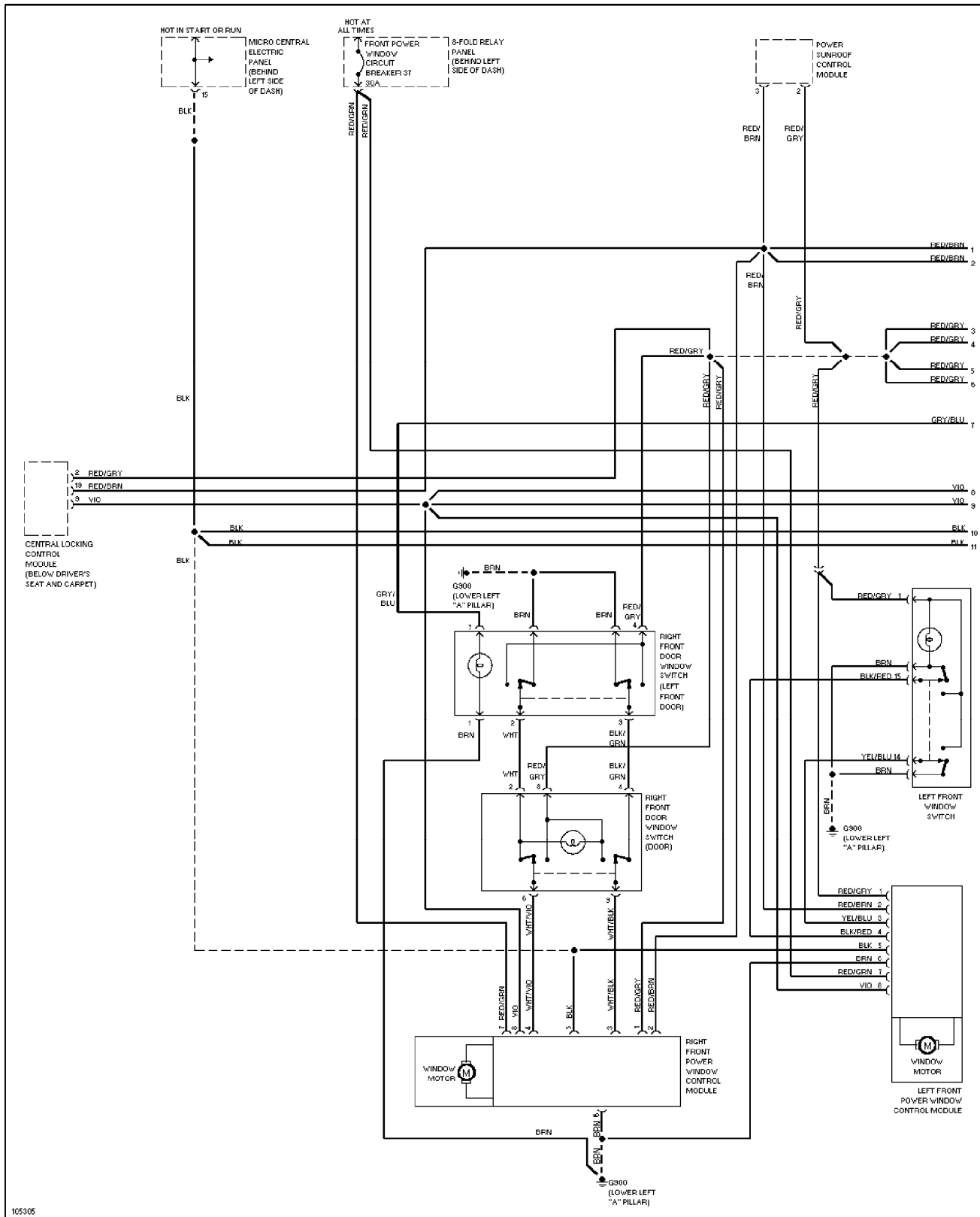


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Radio Circuits, Base Radio W/ CD Changer

1998 Audi A6

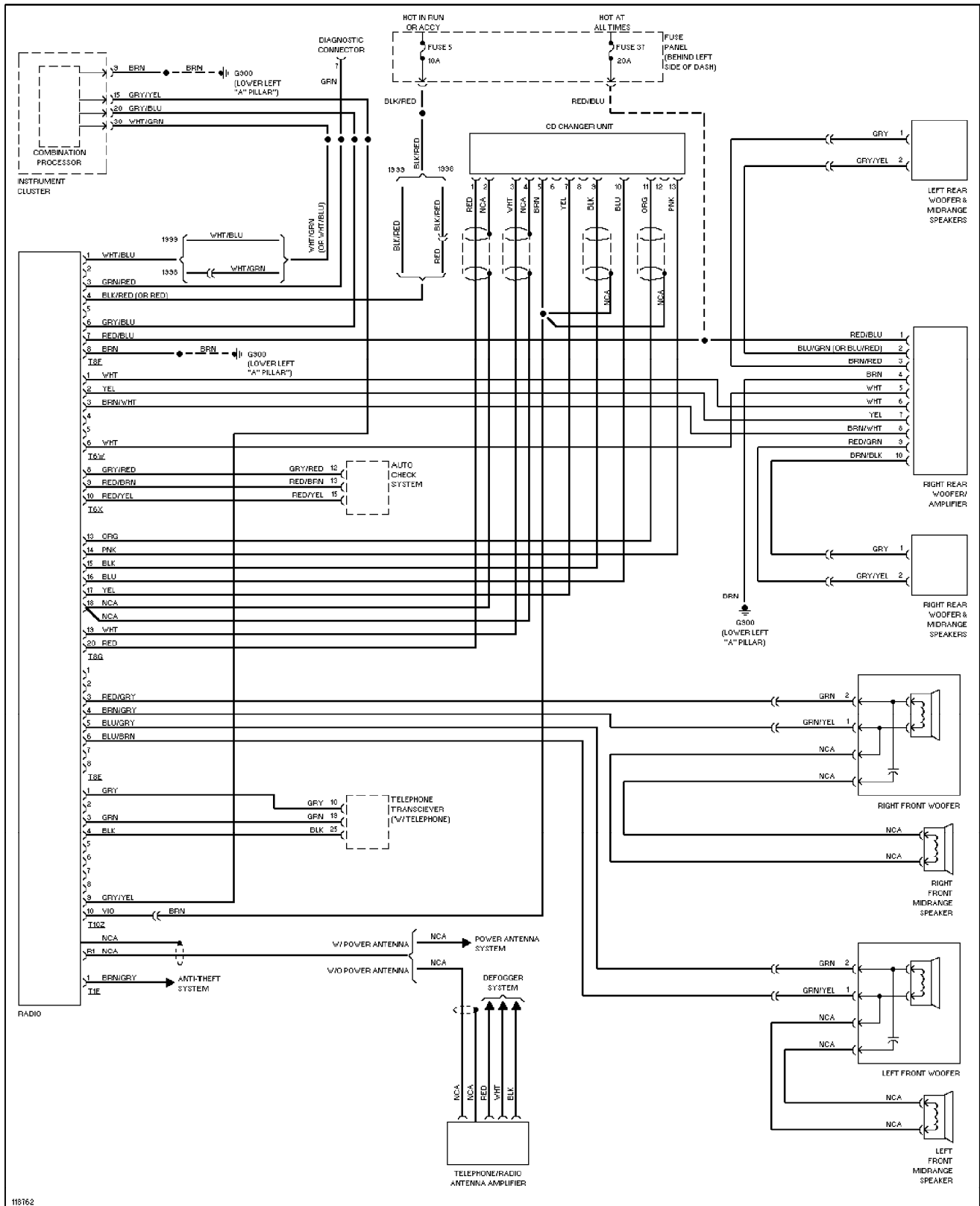


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Radio Circuits, Bose W/ CD Changer


1998 Audi A6

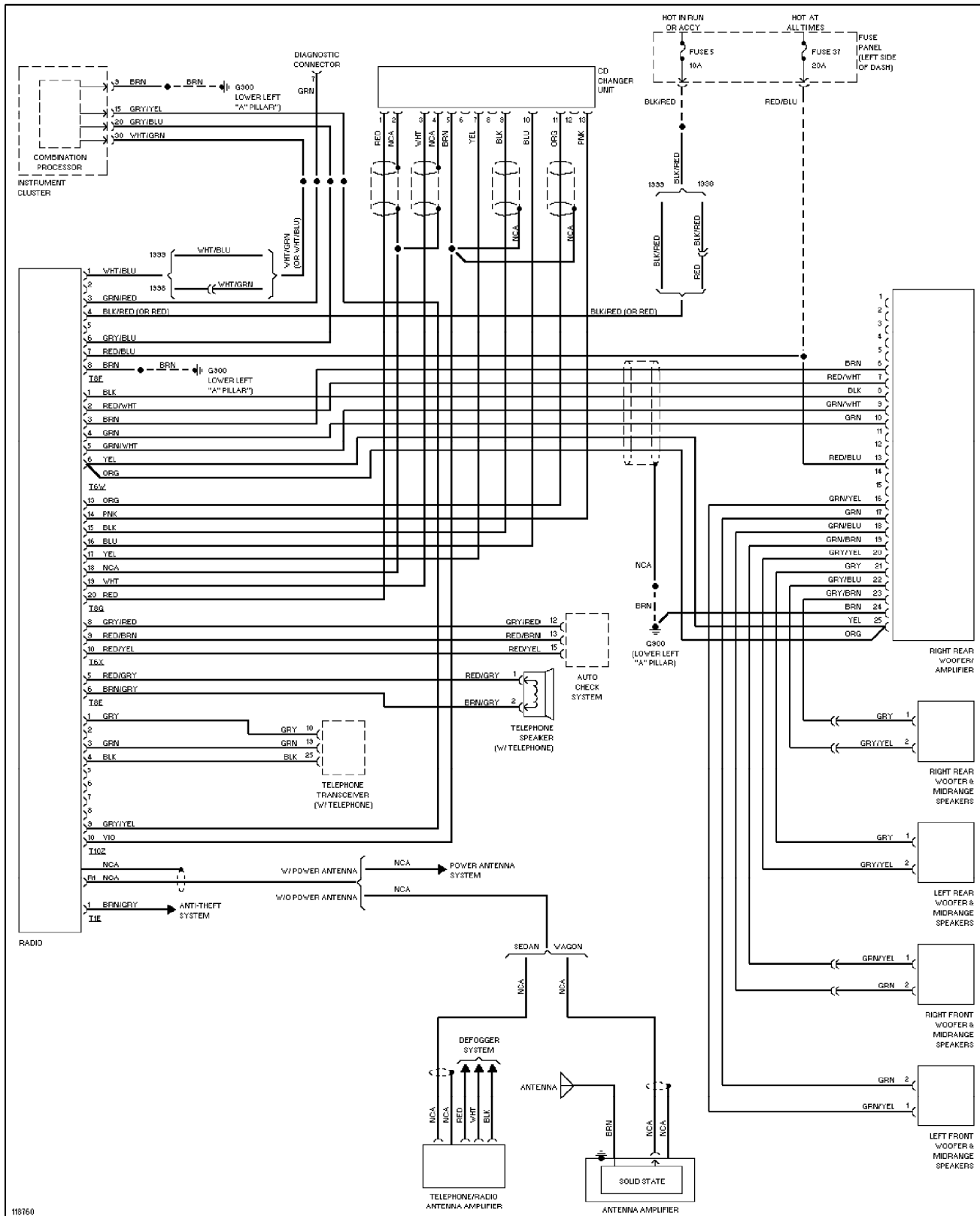

SYSTEM WIRING DIAGRAMS

Radio Circuits, Bose W/O CD Changer


1998 Audi A6

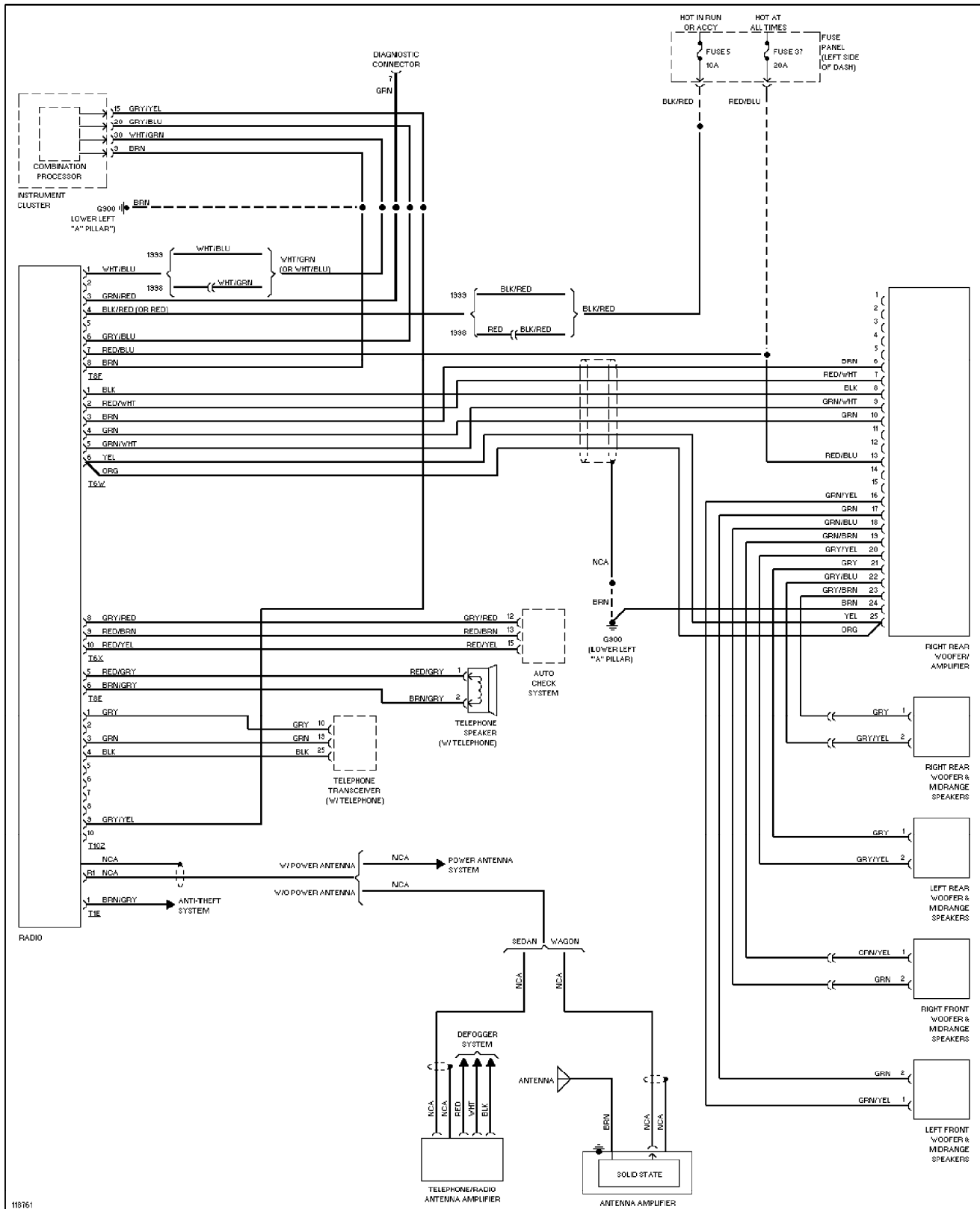

SYSTEM WIRING DIAGRAMS

Shift Interlock Circuit


1998 Audi A6

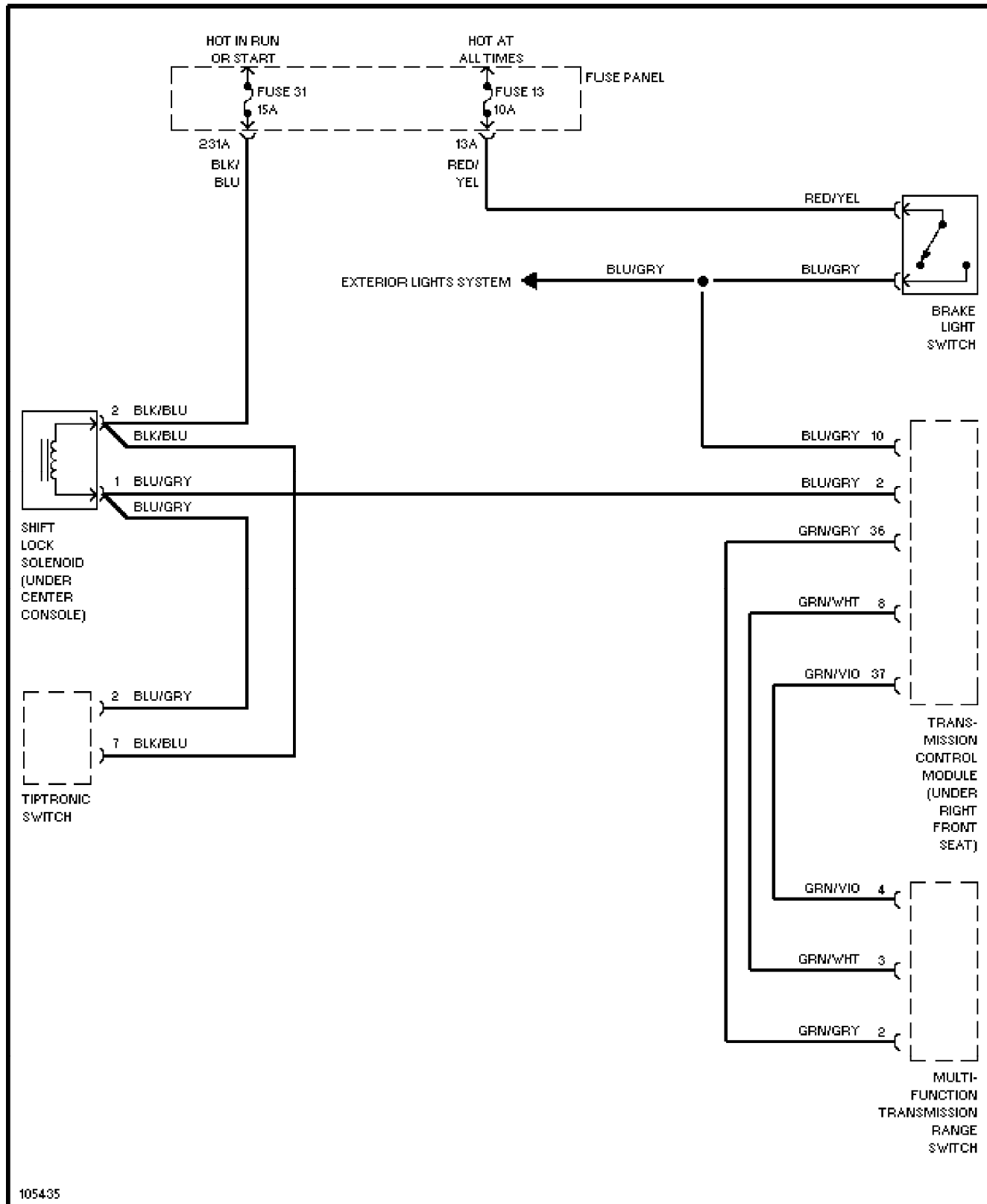

SYSTEM WIRING DIAGRAMS

Charging Circuit


1998 Audi A6

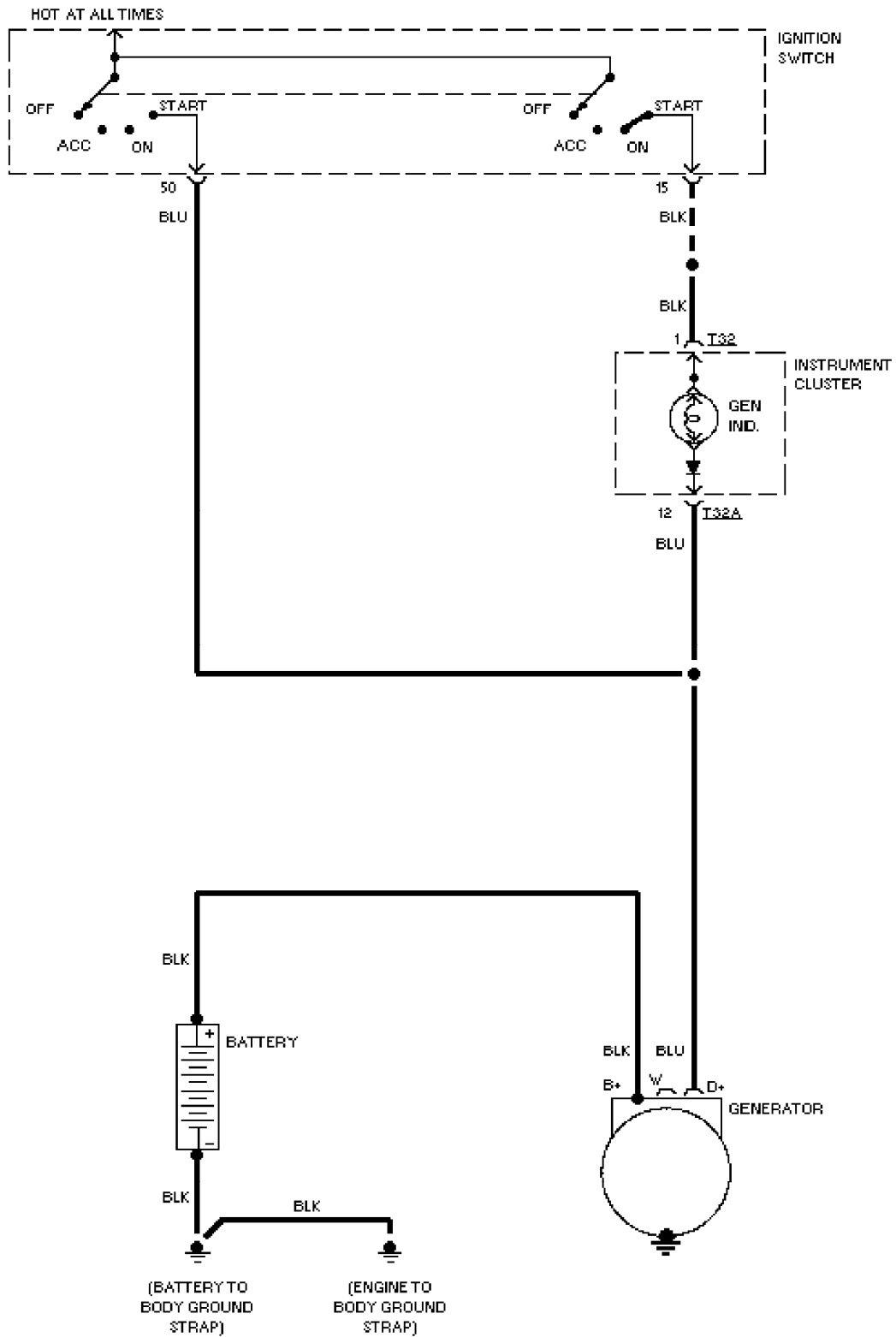

SYSTEM WIRING DIAGRAMS

Starting Circuit


1998 Audi A6

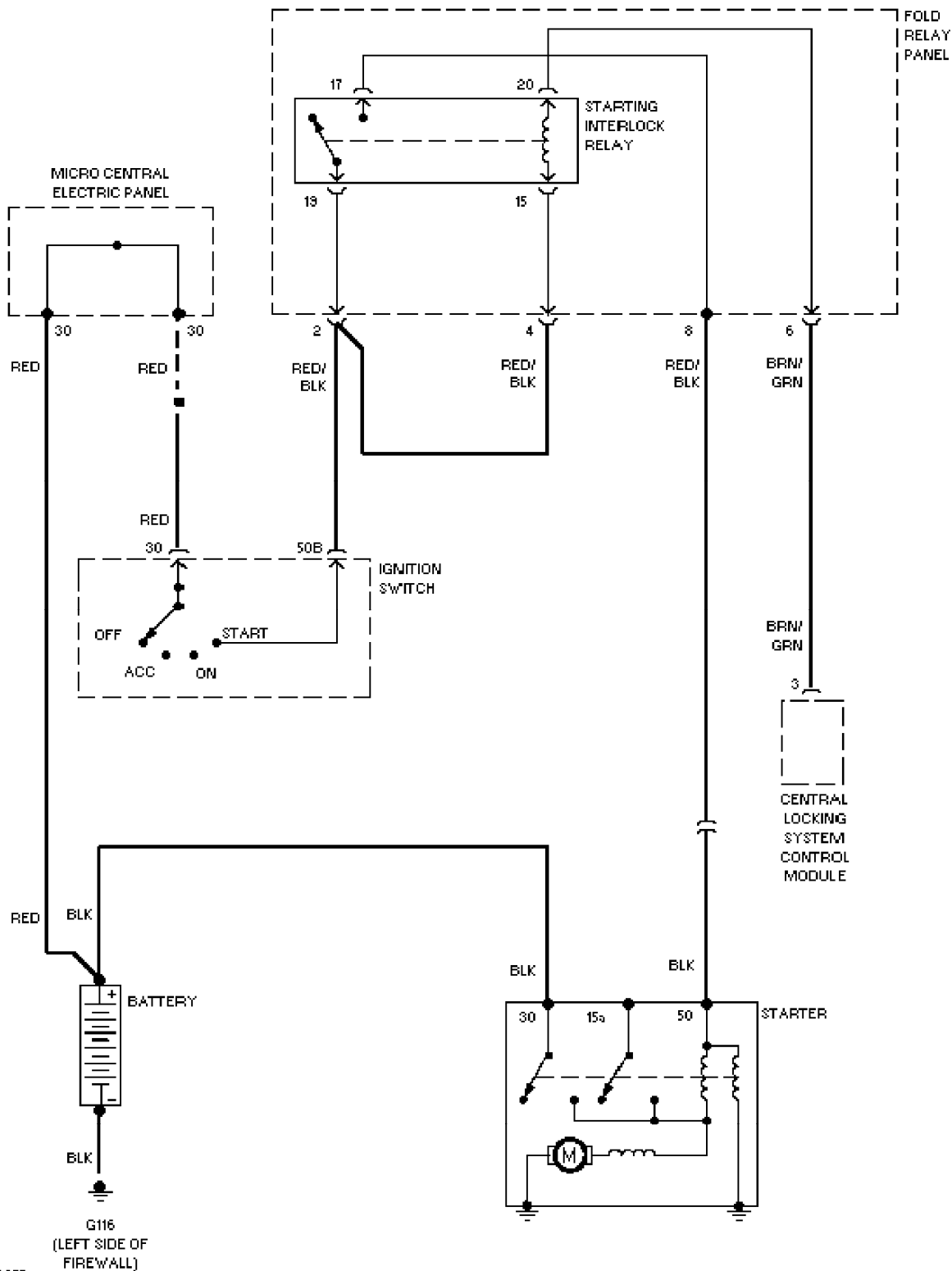

SYSTEM WIRING DIAGRAMS

Supplemental Restraint Circuit


1998 Audi A6

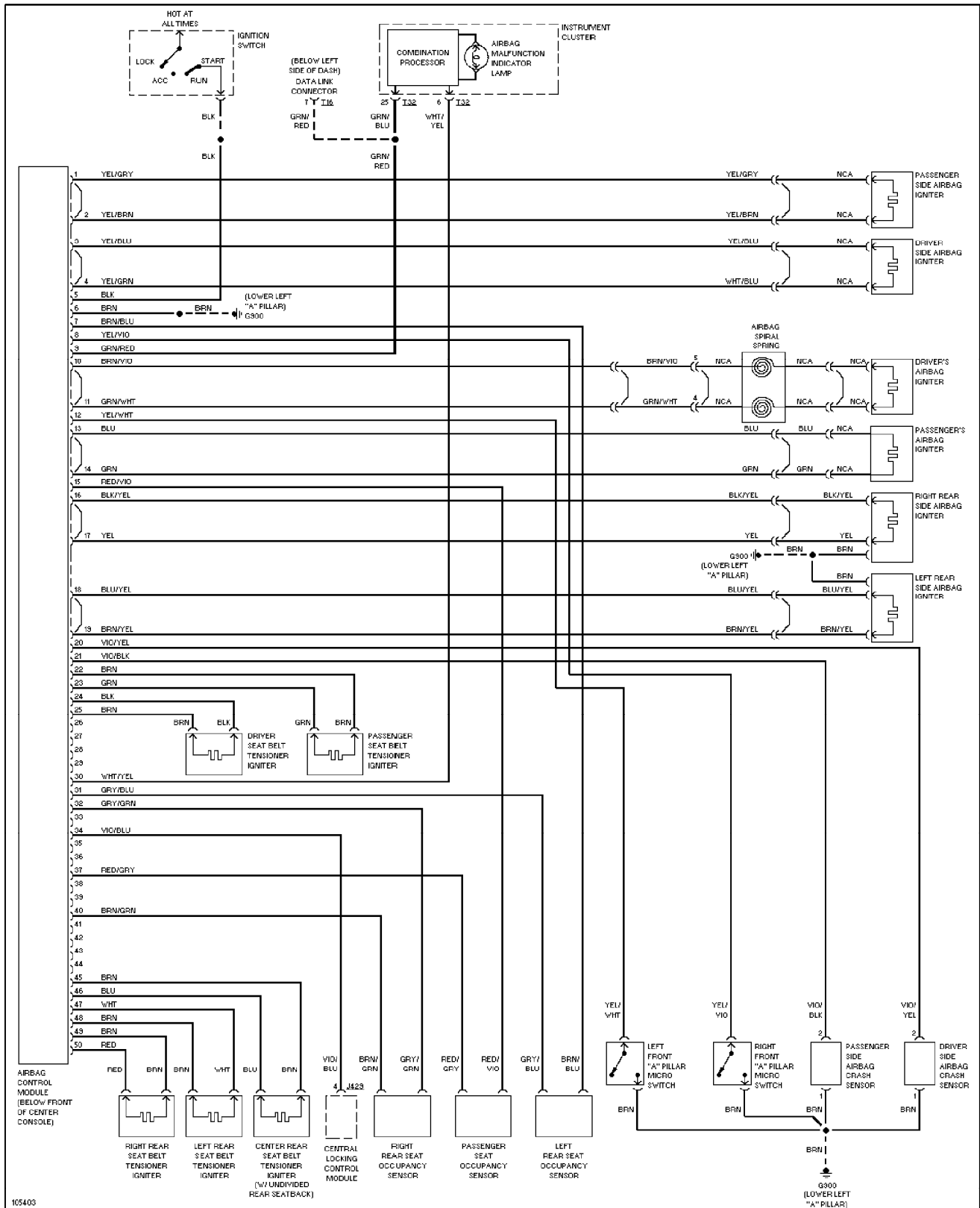

SYSTEM WIRING DIAGRAMS

AT Circuit


1998 Audi A6

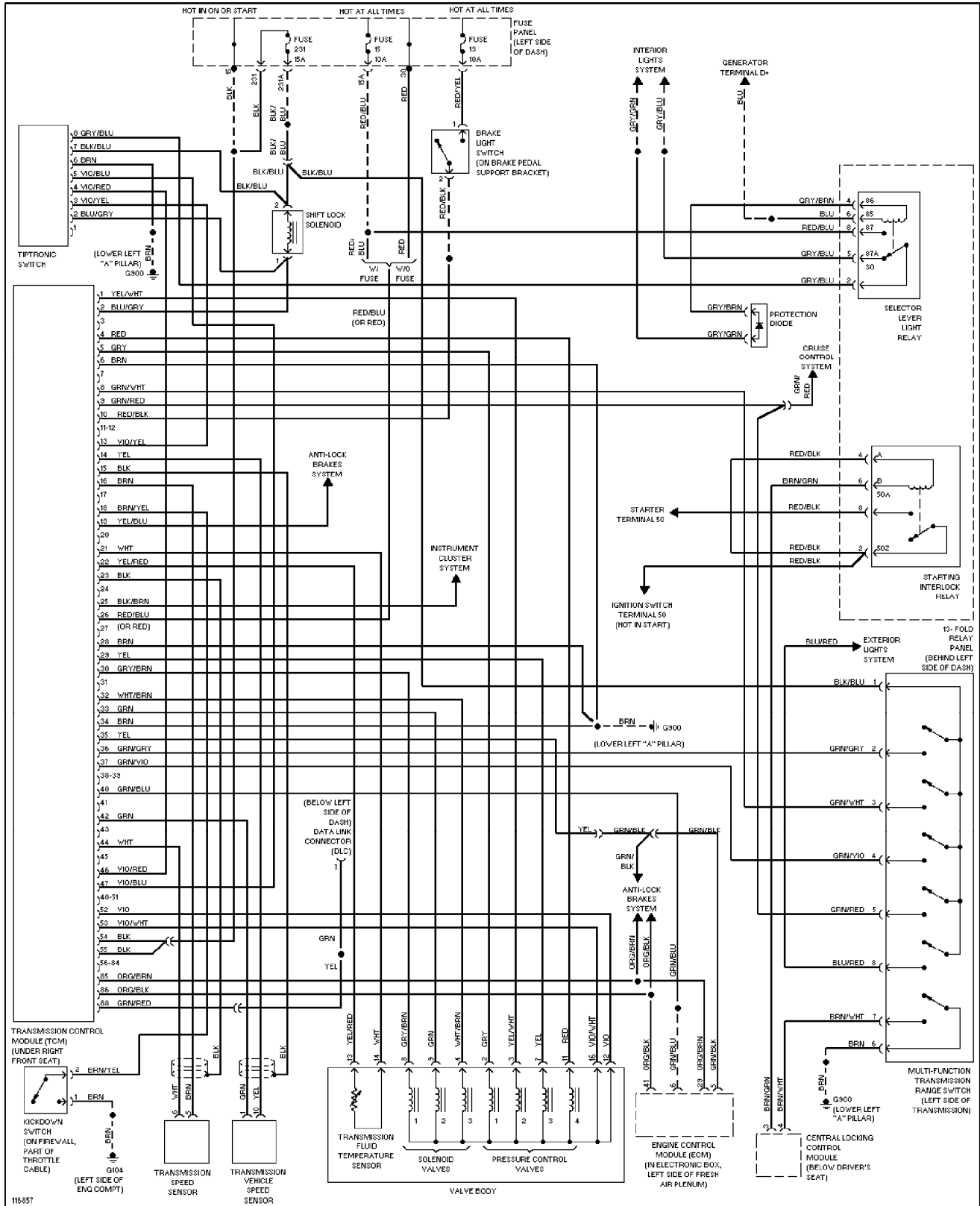

SYSTEM WIRING DIAGRAMS

Power Door Lock Circuit (2 of 2)


1998 Audi A6

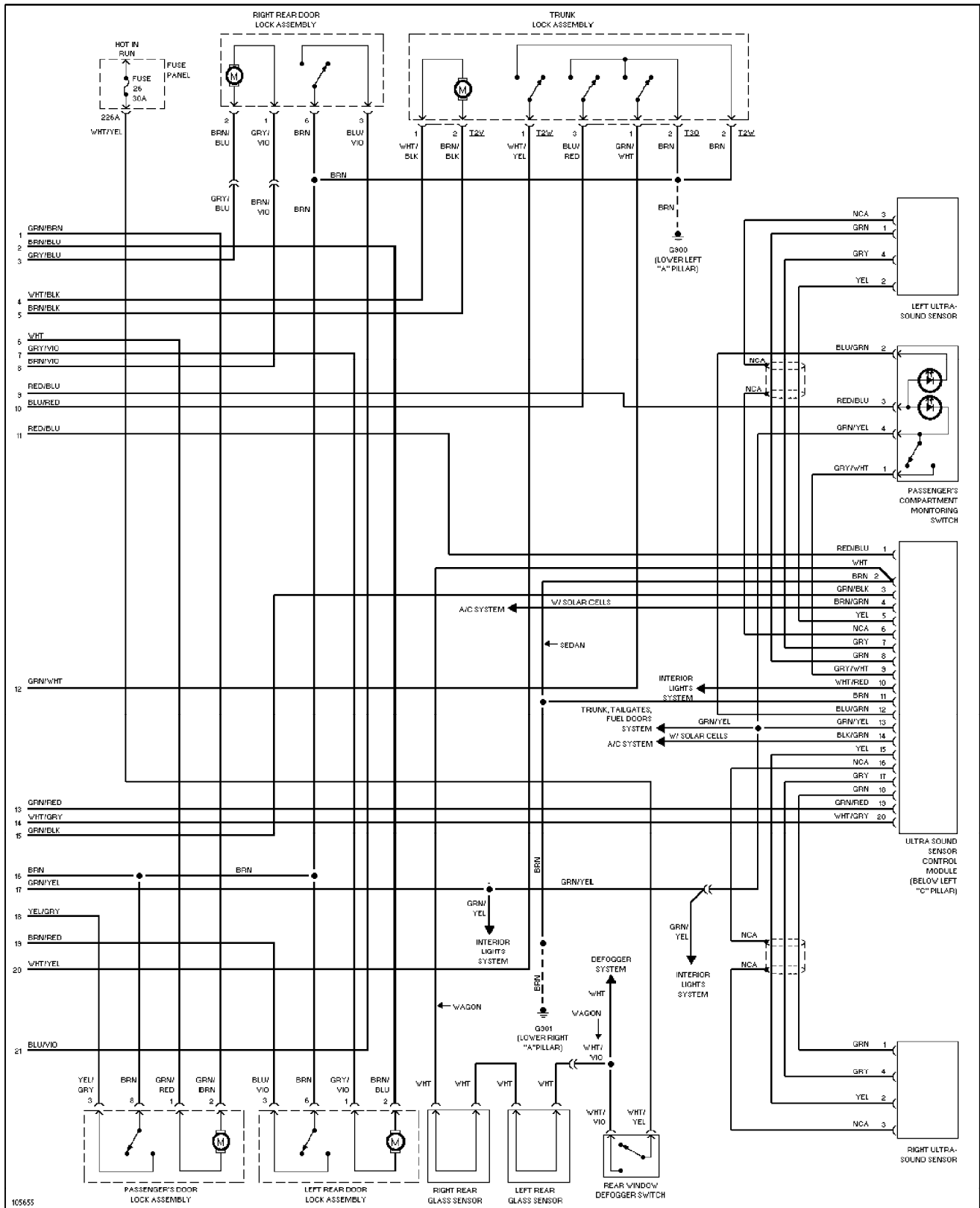

SYSTEM WIRING DIAGRAMS

Headlamps/Fog Lamps Circuit, W/ DRL


1998 Audi A6

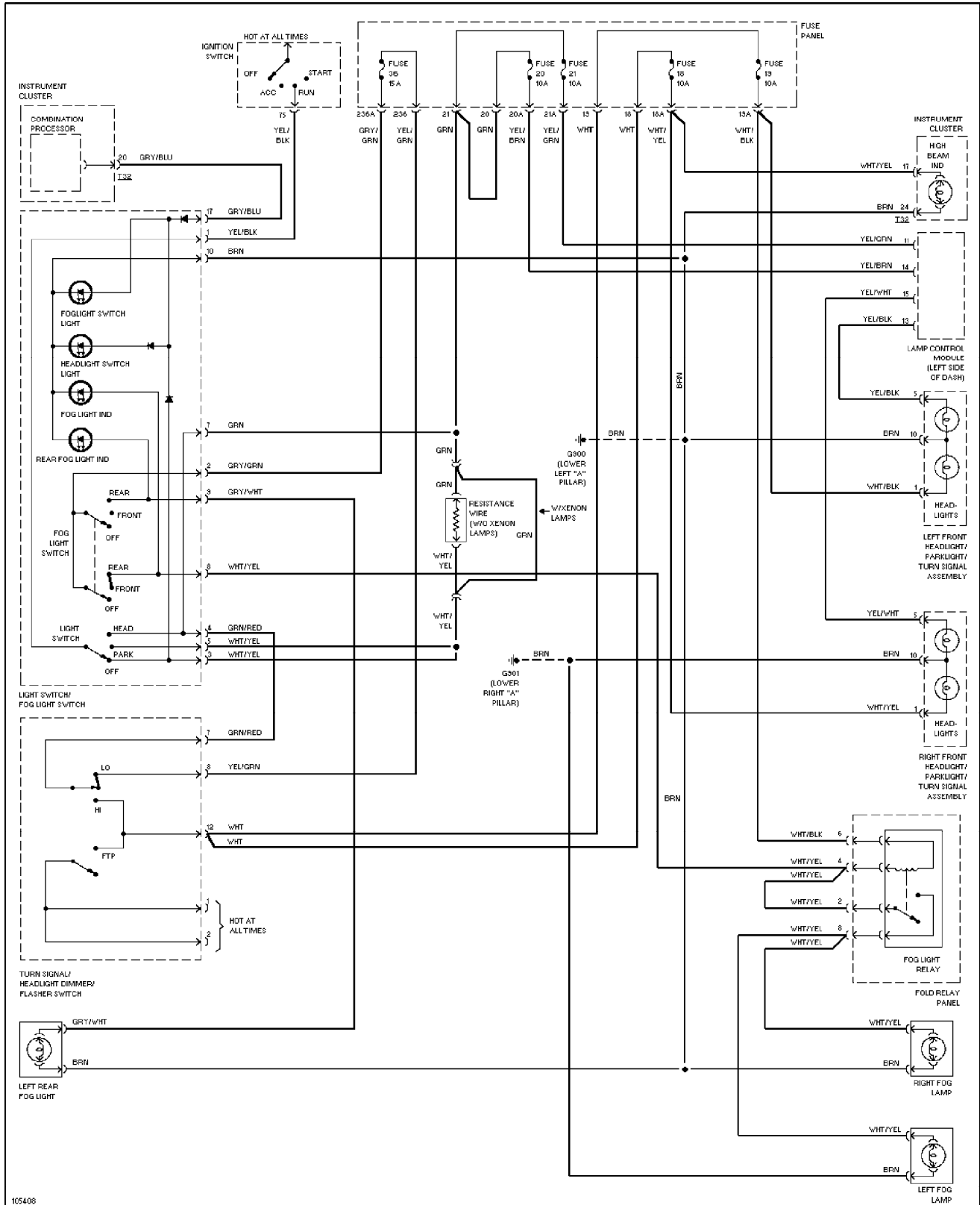

SYSTEM WIRING DIAGRAMS

Headlamps/Fog Lamps Circuit, W/O DRL


1998 Audi A6

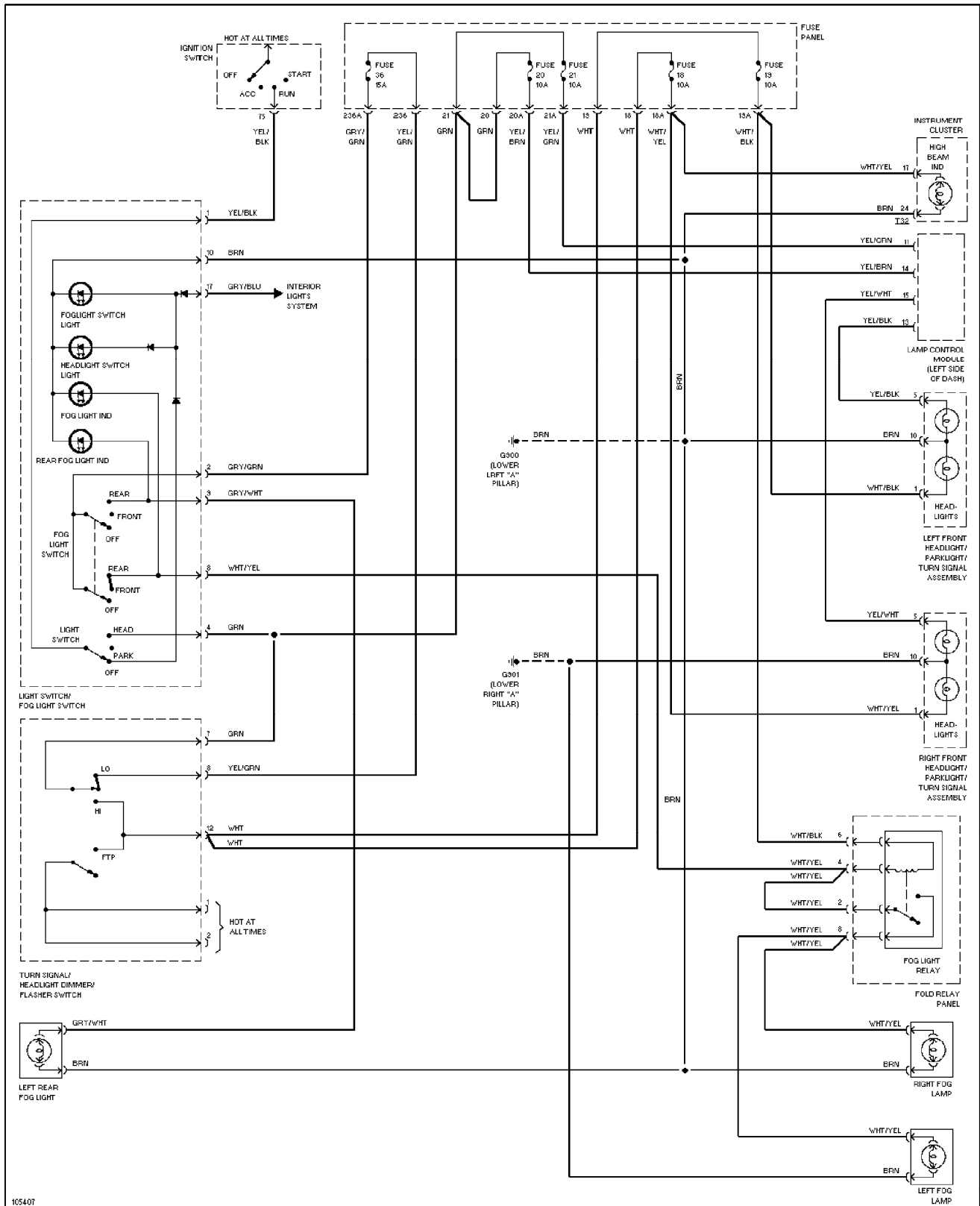

SYSTEM WIRING DIAGRAMS

Horn Circuit


1998 Audi A6

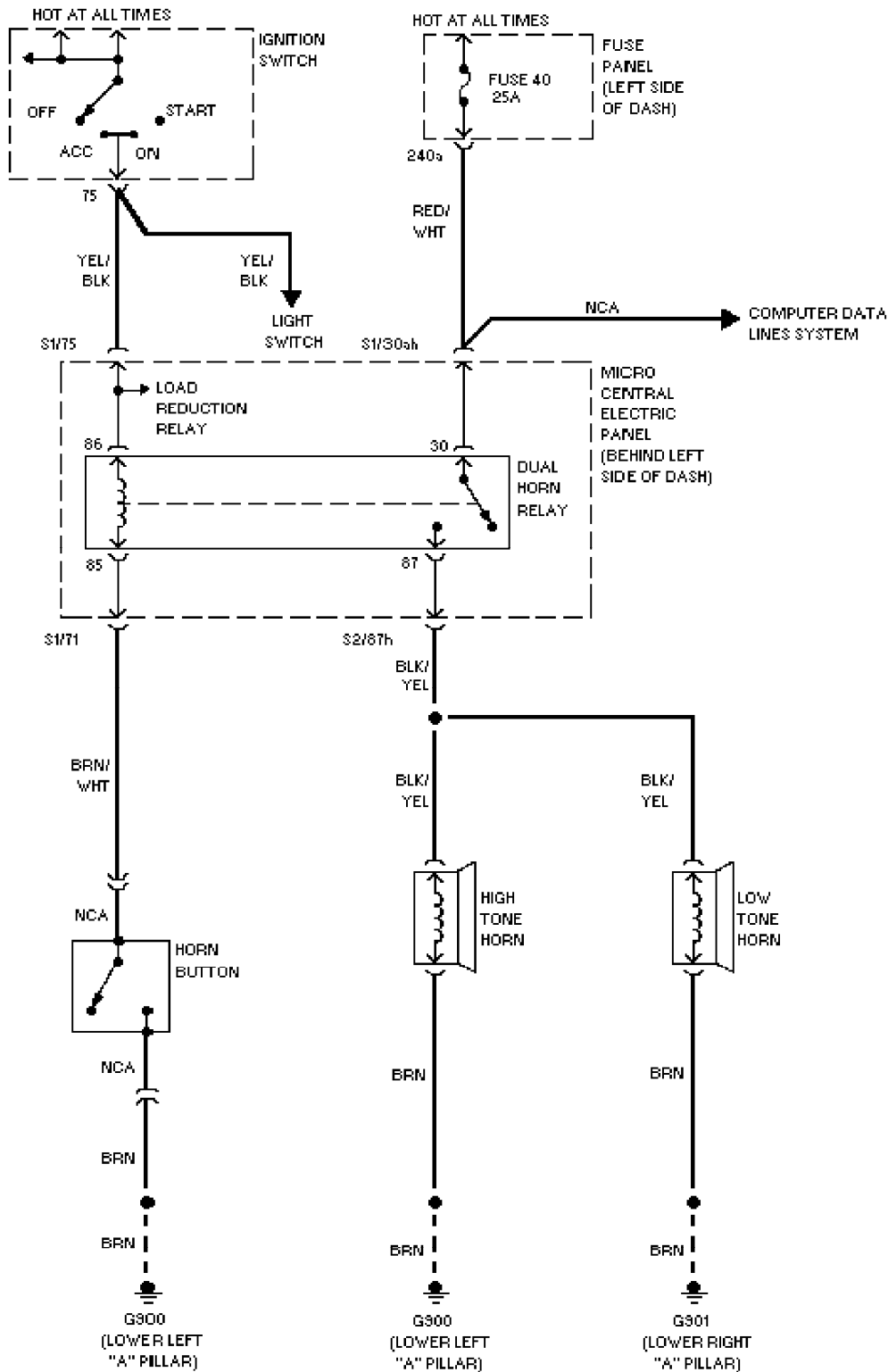

SYSTEM WIRING DIAGRAMS

Auto Check System

1998 Audi A6

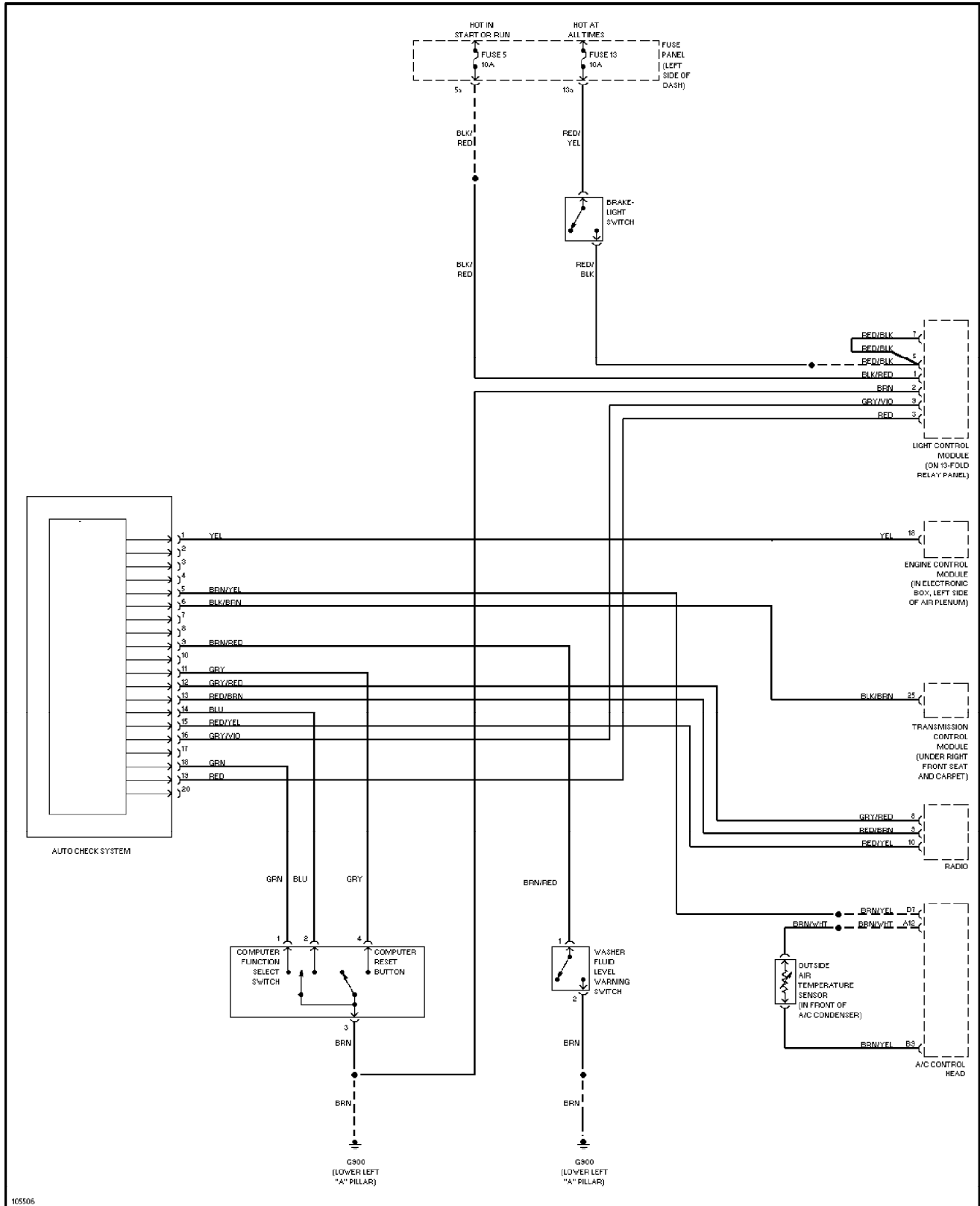


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Interior Light Circuit (1 of 3)

1998 Audi A6

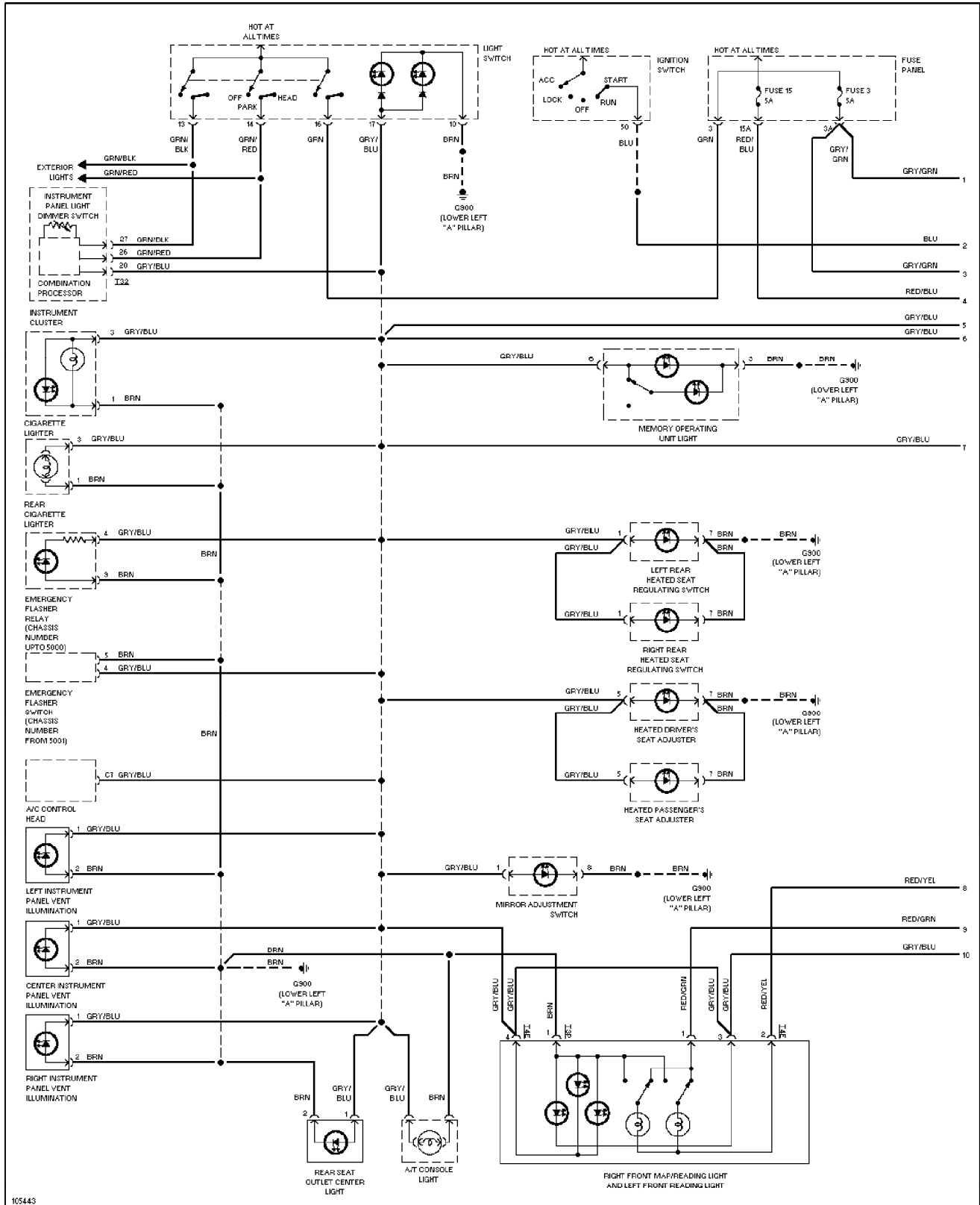


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Interior Light Circuit (3 of 3)


1998 Audi A6

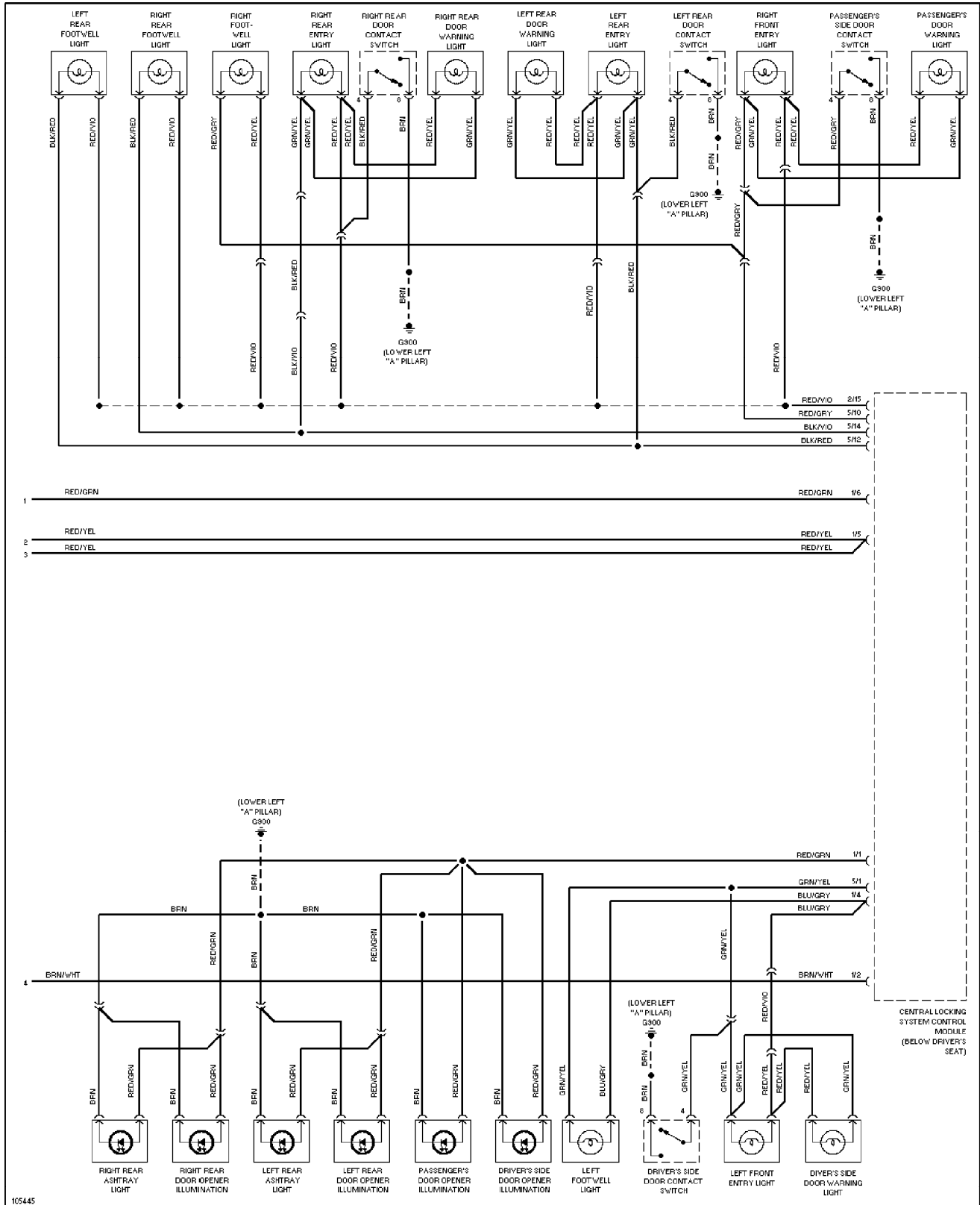

SYSTEM WIRING DIAGRAMS

Driver's Memory Seat Circuit

1998 Audi A6

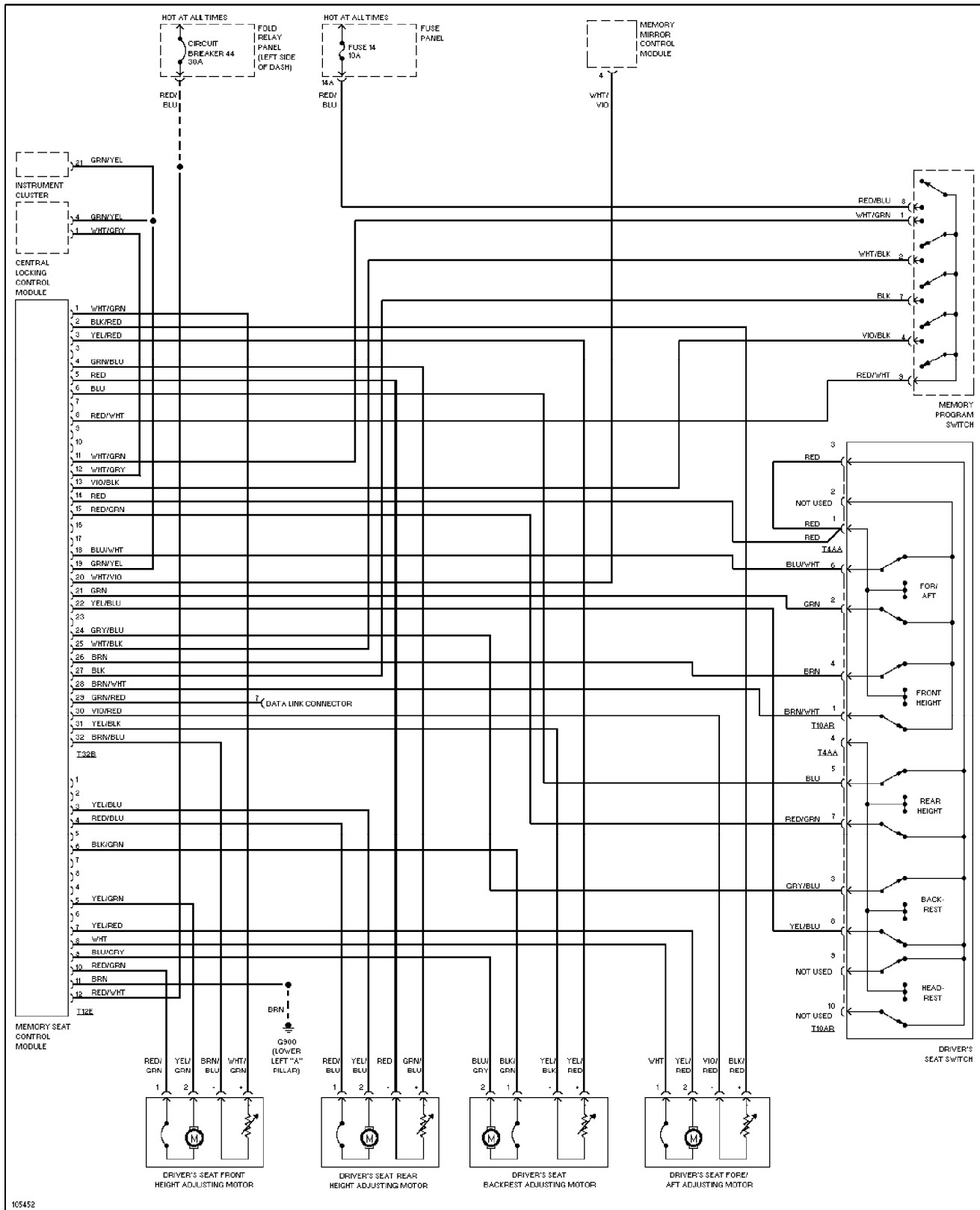


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Power Antenna Circuit

1998 Audi A6

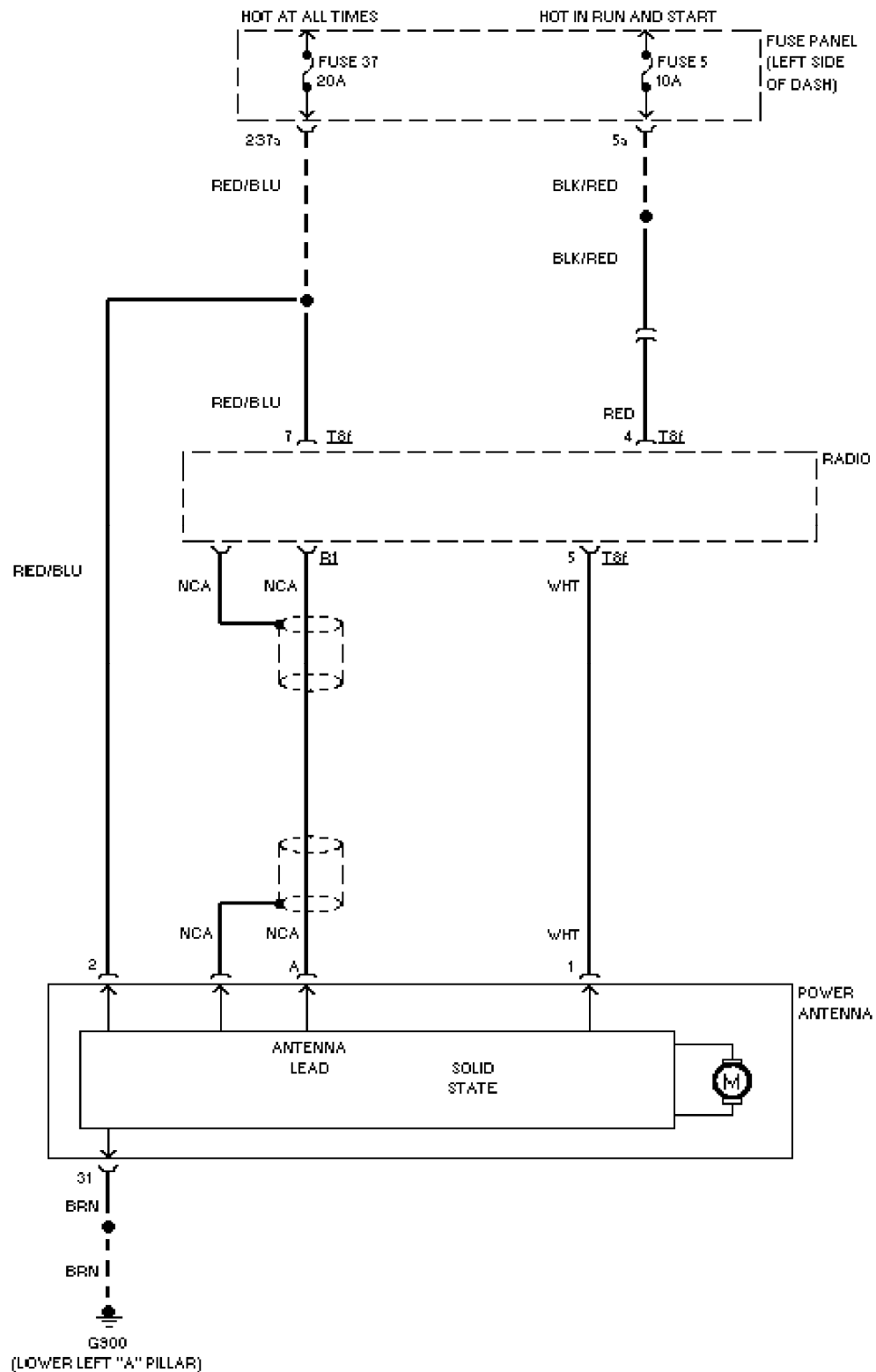


1998 Audi A6



SYSTEM WIRING DIAGRAMS

Power Distribution Circuit (2 of 3)

1998 Audi A6

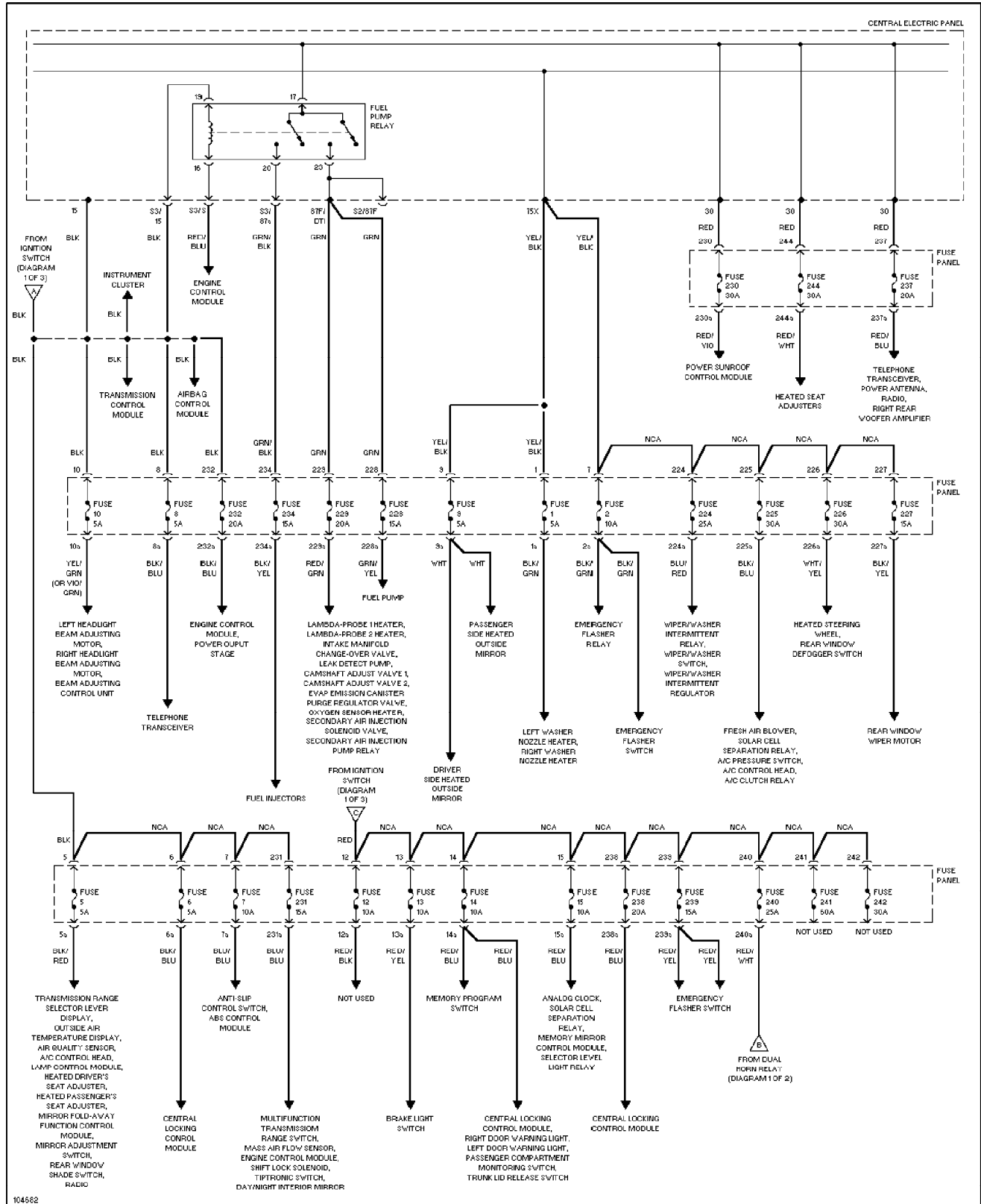

SYSTEM WIRING DIAGRAMS

Power Distribution Circuit (3 of 3)

1998 Audi A6

